

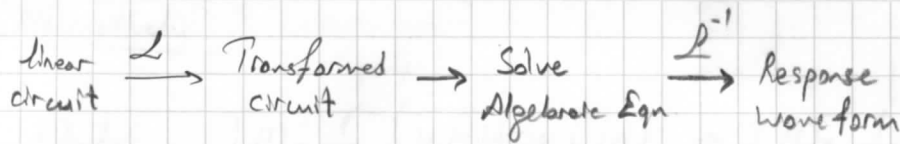
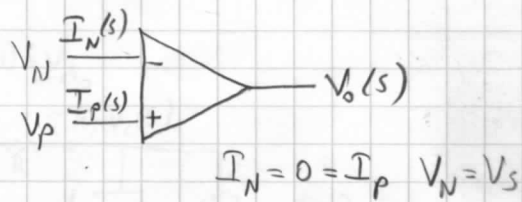
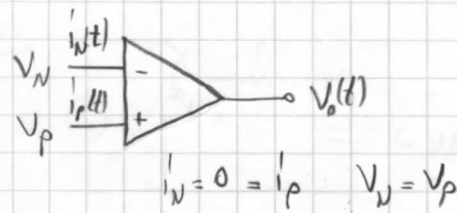
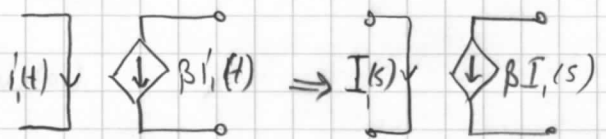
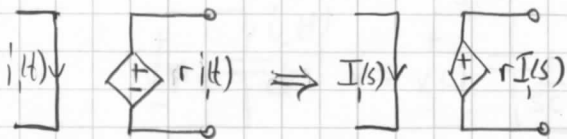


Ch 10 S-Domain Circuit Analysis

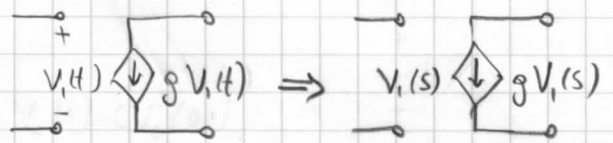


Voltage Source $V(t) \leftrightarrow V(s)$

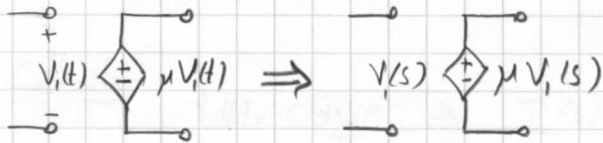Current Source $i(t) \leftrightarrow I(s)$




Resistor

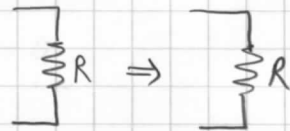$V_R(t) = R i_R(t) \rightarrow V_R(s) = R I_R(s)$




Inductor

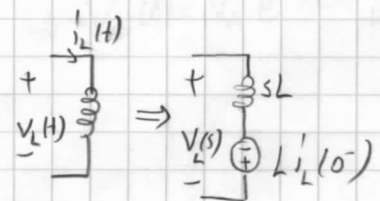$V_L(t) = L \frac{di_L}{dt} \Rightarrow V_L(s) = L s I_L(s) - L i_L(0^-) + \int_{0^-}^t i_L(\tau) d\tau$




Capacitor

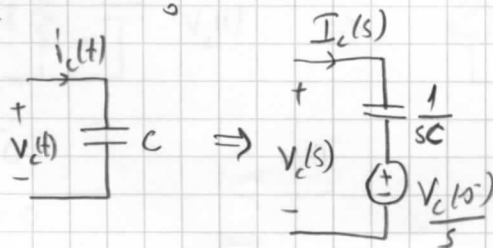$V_C(t) = \frac{1}{C} \int_0^t i_C(\tau) d\tau + V_C(0^-) \Rightarrow V_C(s) = \frac{1}{C} \frac{I_C(s)}{s} + \frac{V_C(0^-)}{s}$




Alternatively

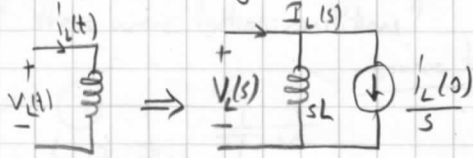Inductor $i_L(t) = \frac{1}{L} \int_0^t V_L(\tau) d\tau + i_L(0) \Rightarrow I_L(s) = \frac{1}{L} \frac{V_L(s)}{s} + \frac{i_L(0)}{s}$




Capacitor
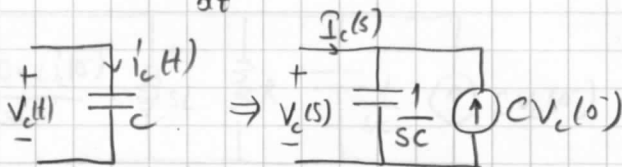
$$i_C(t) = C \frac{dV_C(t)}{dt} \Rightarrow I_C(s) = Cs V_C(s) - CV_C(0)$$




ex

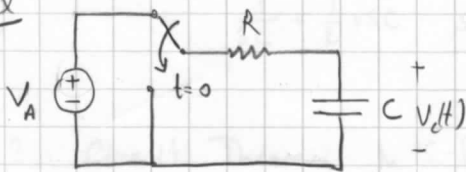

$V_C(t) = ?$

$$V_C(0) = V_A$$

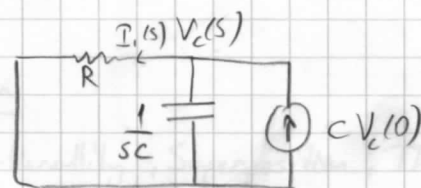


$$-CV_C(0) + sC V_C(s) + \frac{V_C(s)}{R} = 0$$

$$V_C(s) = \frac{CV_C(0)}{sC + \frac{1}{R}} = \frac{V_A}{s + \frac{1}{RC}} \Rightarrow V_C(t) = V_A e^{-\frac{1}{RC}t} u(t)$$

10.2 Basic Circuit Analysis in s-Domain

(It is the same as resistive circuits)

ex

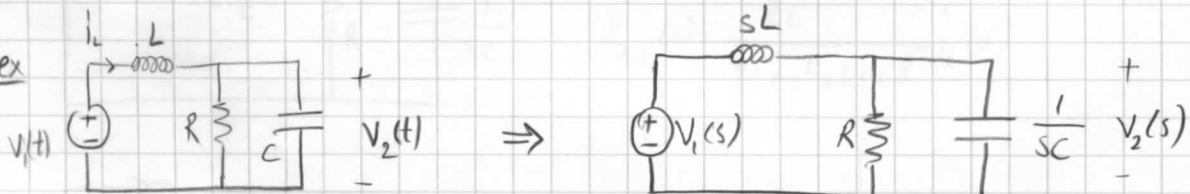

$$i_L(0) = 0$$

$$V_C(0) = 0$$



$$Z_{EQ1} = \frac{1}{\frac{1}{R} + sC} = \frac{R}{sRC + 1}$$

find eq impedance and $V_2(s)$

$$Z_{EQ} = sL + \frac{R}{1 + sRC} = \frac{s^2 RC + sL + R}{1 + sRC}$$




$$V_2(s) = V_1(s) \frac{R}{1+sRC} = V_1(s) \frac{R}{RLCs^2 + Ls + R}$$

What if there were initial conditions?

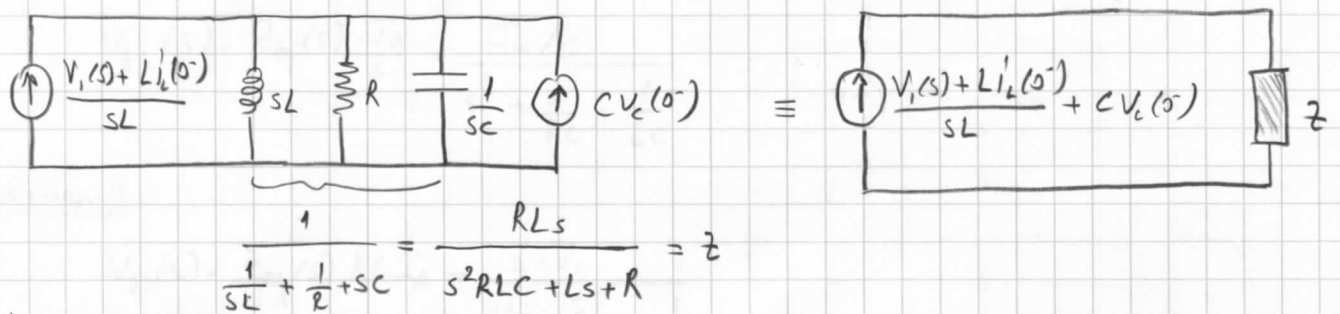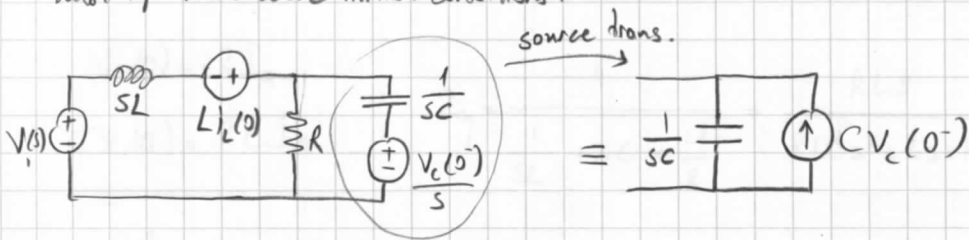

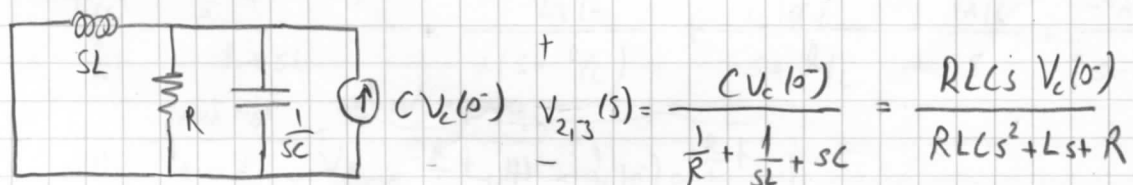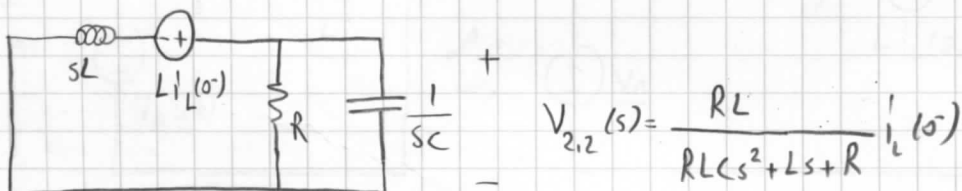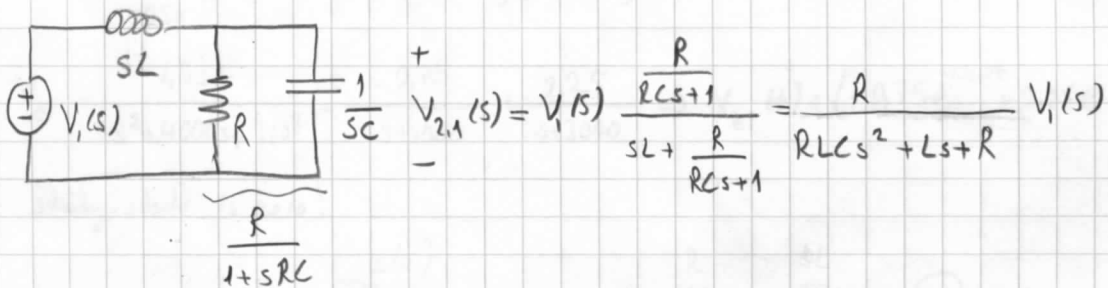
10.3. Circuit Theorems in s-Domain

(Same as resistive circuits: Proportionality, Superposition, Thevenin & Norton Eqv.)



$$V_2(s) = \frac{R}{RLCs^2 + Ls + R} V_1(s) + \frac{RL}{RLCs^2 + Ls + R} i'_L(0^-) + \frac{RLCs}{RLCs^2 + Ls + R} V_c(0^-)$$

zero-state response
zero-input response

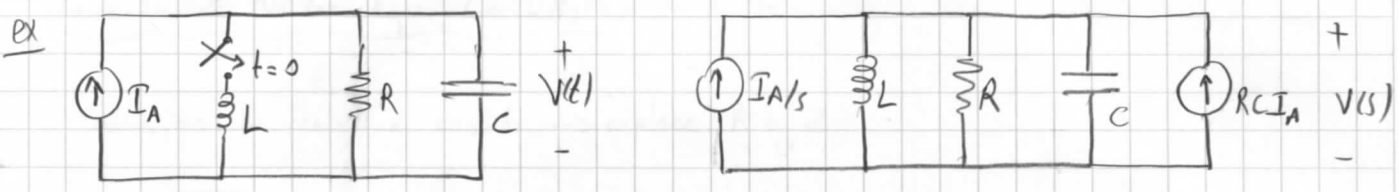

$$V_c(s) = R I_A$$

$$C V_c(0) = RC I_A$$

$$Z_{eq} = \frac{1}{\frac{1}{sL} + sC + \frac{1}{R}} = \frac{RLs}{RLCs^2 + Ls + R}$$

zero-state response

$$V_{zs}(s) = Z_{eq}(s) \frac{I_A}{s} = \frac{I_A / C}{s^2 + \frac{s}{RC} + \frac{1}{LC}}$$

zero-input

$$V_{zi}(s) = Z_{eq}(s) RC I_A = \frac{s R I_A}{s^2 + \frac{s}{RC} + \frac{1}{LC}}$$


$I_A = 1 \text{ mA}$, $L = 2 \text{ H}$, $R = 1.5 \text{ k}\Omega$, $C = \frac{1}{6} \mu\text{F}$

$$V_{zs} = \frac{6000}{s^2 + \frac{s}{250} + 3 \cdot 10^6} = \frac{6000}{(s+1000)(s+3000)} = \frac{3}{s+1000} - \frac{3}{s+3000} \Rightarrow V_{zs}(t) = (3e^{-1000t} - 3e^{-3000t}) u(t)$$

$$V_{zi} = \frac{1.5s}{s^2 + 4000s + 3 \cdot 10^6} = \frac{-0.75}{s+1000} + \frac{2.25}{s+3000} \Rightarrow V_{zi}(t) = (-0.75e^{-1000t} + 2.25e^{-3000t}) u(t)$$

steady-state is zero!

example

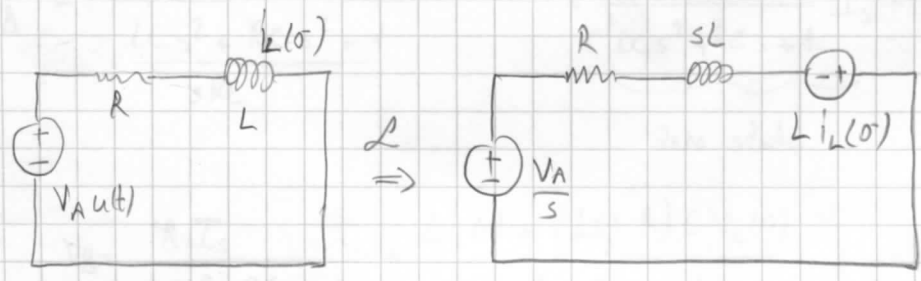


$$I(s) = \frac{\frac{V_A}{s} + L i_L(0)}{R + sL} = \frac{V_A / L}{s(s + R/L)} + \frac{i_L(0)}{s + R/L} = \frac{V_A / R}{s} + \frac{-V_A / R}{s + R/L} + \frac{i_L(0)}{s + R/L}$$

$$i(t) = \underbrace{\frac{V_A}{R} u(t)}_{\text{forced resp. zero-state resp.}} - \underbrace{\frac{V_A}{R} e^{-\frac{R}{L}t} u(t)}_{\text{natural response}} + \underbrace{i_L(0) e^{-\frac{R}{L}t} u(t)}_{\text{zero-input resp.}}$$


zero-state resp. has both forced & natural resp. components.

Thevenin & Norton Eqv. Circuits

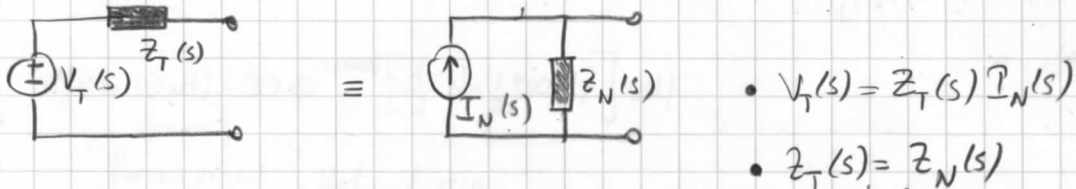Same as in resistive circuits \rightarrow replace R by Z



example

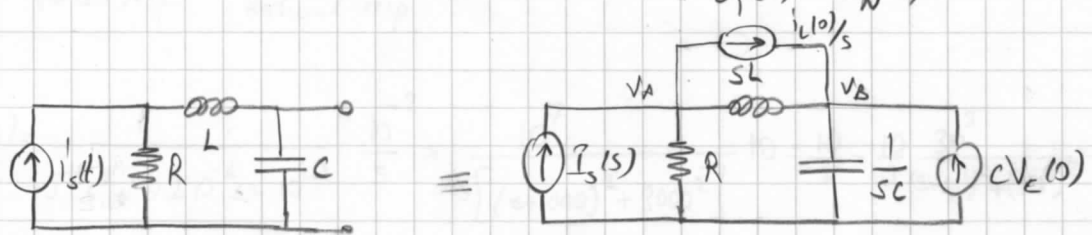

$$\text{Node A: } \frac{V_A}{R} + \frac{i_L(0)}{s} + \frac{V_A - V_B}{sL} - I_s(s) = 0$$

$$\text{Node B: } -\frac{i_L(0)}{s} + \frac{V_B - V_A}{sL} + sC V_B - C V_c(0) = 0$$

$$\begin{bmatrix} \frac{1}{R} + \frac{1}{sL} & -\frac{1}{sL} \\ -\frac{1}{sL} & \frac{1}{sL} + sC \end{bmatrix} \begin{bmatrix} V_A \\ V_B \end{bmatrix} = \begin{bmatrix} I_s(s) - i_L(0)/s \\ C V_c(0) + i_L(0)/s \end{bmatrix}$$

$$V_A = \frac{\Delta_A}{\Delta} = \frac{\frac{LCs^2+1}{sL} I_s + \frac{-LCs i_L(0) + C V_c(0)}{sL}}{\frac{LCs^2 + RCs^2 + 1}{sRL}} = \underbrace{\frac{RLCs^2+1}{LCs^2+RCs+1}}_{\text{zero state}} I_s + \underbrace{\frac{-RLCs i_L(0) + RC V_c(0)}{LCs^2+RCs+1}}_{\text{zero input}}$$

$$\text{similarly: } V_B = \underbrace{\frac{R I_s}{LCs^2+RCs+1}}_{\text{zero state}} + \underbrace{\frac{L i_L(0) + (Ls+R) C V_c(0)}{LCs^2+RCs+1}}_{\text{zero input}}$$

Numerical values $R = 1 \text{ k}\Omega$, $L = 0,5 \text{ H}$, $C = 0,2 \mu\text{F}$, $i_s(t) = 10 u(t) \text{ mA}$

$$V_A(s) = \frac{10^{-7} s^2 + 1}{10^{-3} 0,5 0,2 10^6 s^2 + 0,2 10^6 s + 10^3} \frac{10^{-2}}{s} = 10 \frac{s^2 + 10^7}{s [2(s+1000)^2 + 810^6]} = \frac{10}{s} - \frac{20}{3} \frac{3000}{(s+1000)^2 + 3000^2}$$

$$V_A(t) = 10 u(t) - 20 e^{-1000t} \left[\frac{1}{3} \sin(3000t) \right] u(t)$$

forced resp. Natural resp.

$$V_B(s) = \frac{1}{10^{-10} s^2 + 0,2 10^{-6} s + 10^{-3}} \frac{10^{-2}}{s} = \frac{10^7}{s [(s+1000)^2 + 3000^2]} 10 = \frac{10}{s} - \frac{10}{3} \frac{310^3}{(s+10^3)^2 + (310^3)^2} - 10 \frac{s+10^3}{(s+10^3)^2 + (310^3)^2}$$

$$V_B(t) = 10 u(t) - 10 e^{-1000t} \left[\frac{1}{3} \sin 3000t \right] u(t) - 10 e^{-1000t} [\cos 3000t] u(t)$$

Standard form $s^2 + 2\zeta \omega_0 s + \omega_0^2 = s^2 + \frac{R}{L} s + \frac{1}{LC} \Rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$, $\zeta = \frac{R/L}{2 \frac{1}{\sqrt{LC}}} = \frac{R}{2} \sqrt{\frac{C}{L}}$


$\zeta > 1$: overdamped

$\zeta = 1$: critically damped

$\zeta < 1$: underdamped $\Rightarrow s = -\alpha \mp j\beta$ $(s+\alpha)^2 + \beta^2 = 0$

$$s^2 + 2\alpha s + \alpha^2 + \beta^2 = s^2 + 2\zeta \omega_0 s + \omega_0^2$$

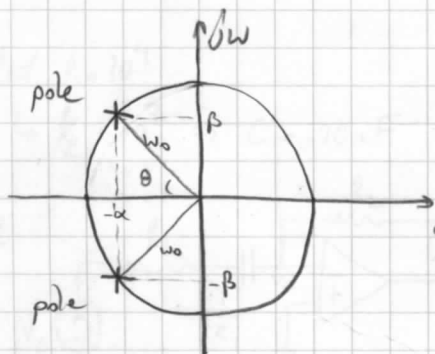
$$\Rightarrow \omega_0^2 = \alpha^2 + \beta^2; \quad \zeta = \frac{\alpha}{\sqrt{\alpha^2 + \beta^2}}$$



$\cos \theta = \zeta$ & $\omega_0 \rightarrow$ polar coordinates

$\alpha, \beta \rightarrow$ rectangular coordinates.

example

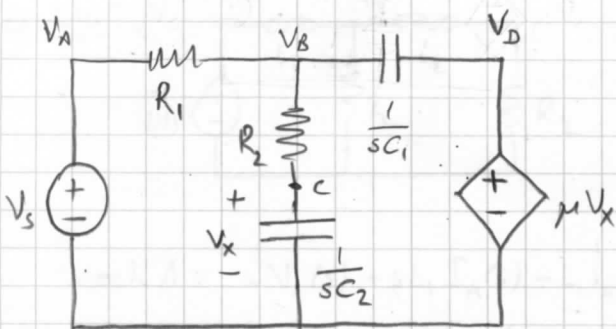

Node Analysis

① Assign node voltages

② From voltage sources

$$V_A(s) = V_s(s)$$

$$V_D(s) = \mu V_x$$

③ For dependent sources substitute node voltages

$$V_D(s) = \mu V_x = \mu V_C(s)$$

④ Write KCL eqns at other nodes.

Node B: $\frac{V_B - V_A}{R_1} + \frac{V_B - V_C}{R_2} + \frac{V_B - \mu V_C}{1/sC_1} = 0$

Node C: $\frac{V_C}{1/sC_2} + \frac{V_C - V_B}{R_2} = 0$

$$\begin{bmatrix} sC_1 + \frac{1}{R_1} + \frac{1}{R_2} & -\mu sC_1 - \frac{1}{R_2} \\ -\frac{1}{R_2} & sC_2 + \frac{1}{R_2} \end{bmatrix} \begin{bmatrix} V_B \\ V_C \end{bmatrix} = \begin{bmatrix} V_s/R_1 \\ 0 \end{bmatrix}$$

design $\omega_0 = 1000 \text{ rad/s}$, $\zeta = 0.5$
 $C_1 = C_2 = C$, $R_1 = R_2 = R$

let's find natural poles

$$\Delta(s) = s^2 C^2 + \frac{C}{R} s + \frac{2C}{R} s + \frac{2}{R^2} - \mu \frac{C}{R} s - \frac{1}{R^2}$$


$$\frac{\Delta(s)}{C^2} = s^2 + \frac{(3-\mu)}{RC} s + \frac{1}{R^2 C^2} = s^2 + 2\zeta\omega_0 s + \omega_0^2 \Rightarrow \omega_0 = \frac{1}{RC} = 1000$$

$$\frac{3-\mu}{RC} = 2\zeta\omega_0 = 1000 \Rightarrow \mu = 2$$

let $R = 10^4$

$$\hookrightarrow \frac{1}{C} = 10^7 \Rightarrow C = 100 \text{ nF}$$

example

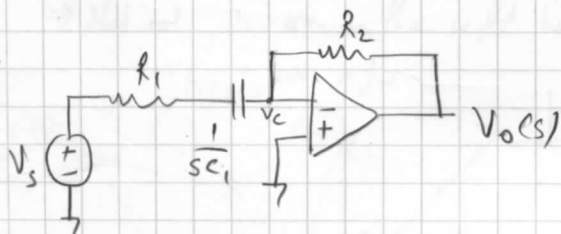

$$V_c = 0$$

$$I_n = 0$$

$$I_p = 0$$

$$\frac{V_c - V_s}{R_1 + \frac{1}{sC_1}} + \frac{V_c - V_o}{R_2} = 0 \Rightarrow V_o(s) = -\frac{sC_1 R_2}{sC_1 R_1 + 1} V_s = -\frac{R_2}{R_1} \frac{s}{s + \frac{1}{R_1 C_1}} V_s$$

If $V_s(t) = u(t) \Rightarrow V_s = \frac{1}{s}$


$$V_o(s) = -\frac{R_2}{R_1} \frac{1}{s + \frac{1}{R_1 C_1}} \Rightarrow V_o(t) = -\frac{R_2}{R_1} e^{-t/R_1 C_1} u(t)$$

Natural pole

Steady-State = 0

Mesh Current Analysis

Example

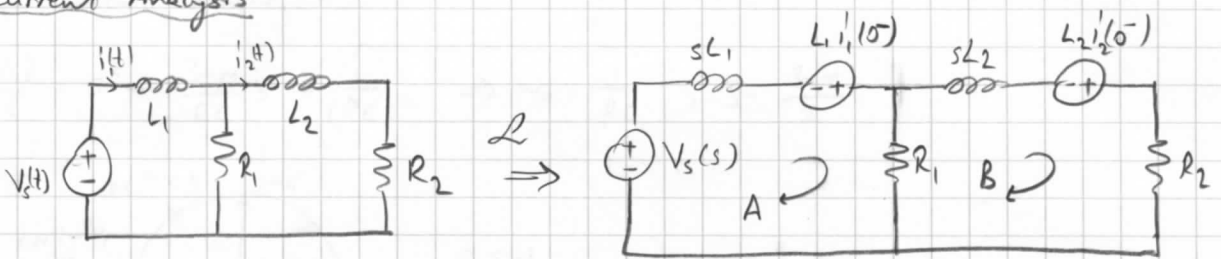

$$\text{mesh A: } -V_s(s) + sL_1 I_A(s) - L_1 i_{L_1}'(0^-) + R_1 (I_A(s) - I_B(s)) = 0$$

$$\text{mesh B: } R_1 (I_B(s) - I_A(s)) + sL_2 I_B(s) - L_2 i_{L_2}'(0^-) + R_2 I_B(s) = 0$$

$$\begin{bmatrix} sL_1 + R_1 & -R_1 \\ -R_1 & R_1 + sL_2 + R_2 \end{bmatrix} \begin{bmatrix} I_A(s) \\ I_B(s) \end{bmatrix} = \begin{bmatrix} V_s(s) + L_1 i_{L_1}'(0^-) \\ L_2 i_{L_2}'(0^-) \end{bmatrix}$$

Summary


$Y(s) = \text{output}$
 → real poles ⇒ exponential, damped ramp
 → complex conjugate ⇒ damped sinusoid.

Natural Poles: zeros of the circuit determinant
 → natural response

Forced Poles: poles of the input
 → forced response


Stability: If natural response decays to zero as $t \rightarrow \infty$

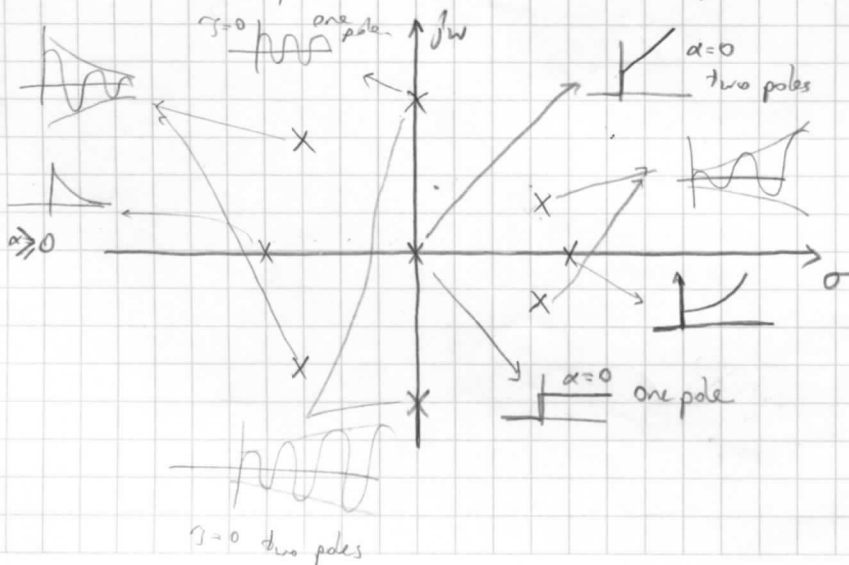⇒ Natural poles are in the left hand plane (LHP)



Op-Amp Circuit Example
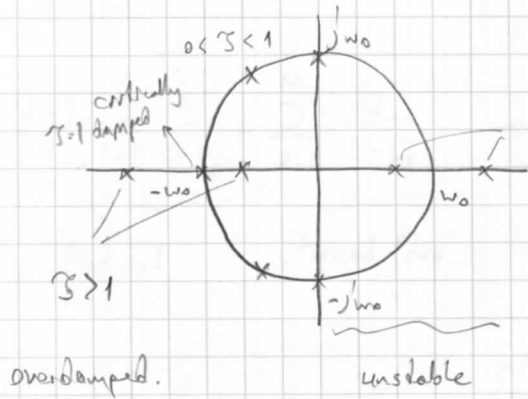
$$\frac{\Delta(s)}{C^2} = s^2 - \frac{3-\mu}{RC} s + \frac{1}{(RC)^2} \Rightarrow \omega_0 = \frac{1}{RC}, \zeta = \frac{3-\mu}{2}$$



In a circuit of positive resistors, capacitors and inductors $\zeta > 0 \Rightarrow$ stable.

However for the above OPAMP circuit

$$\mu > 3 \Rightarrow \zeta < 0 \Rightarrow \text{unstable}$$