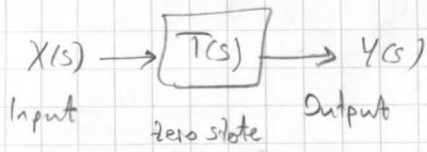


Chapter 11: Network Functions



$$Y(s) = T(s) X(s)$$

\downarrow Natural Poles. \downarrow Forced Poles.

$$Y(s) = \underbrace{\sum_{j=1}^N \frac{k_j}{s-p_j}}_{\text{Natural Poles}} + \underbrace{\sum_{l=1}^M \frac{k_l}{s-p_l}}_{\text{Forced Poles}}$$

$$\Rightarrow y(t) = \underbrace{\sum_{j=1}^N k_j e^{p_j t}}_{\text{Natural response transient}} + \underbrace{\sum_{l=1}^M k_l e^{p_l t}}_{\text{forced response transient + steady state}}$$

{in a stable circuit}

{decay to zero}

{does not decay to zero}

example

$$T(s) = \frac{V_2(s)}{V_1(s)} = \frac{2000(s+2000)}{(s+1000)(s+4000)}$$

$$V_1(t) = (20 + 15e^{-5000t})u(t) \Rightarrow V_1(s) = \frac{20}{s} + \frac{15}{s+5000} = \frac{35s + 10^5}{s(s+5000)}$$

$$V_2(s) = \frac{10^4(s+2 \cdot 10^3)(7s+2 \cdot 10^4)}{s(s+10^3)(s+4 \cdot 10^3)(s+5 \cdot 10^3)} = \frac{k_1}{s+10^3} + \frac{k_2}{s+4 \cdot 10^3} + \frac{k_3}{s} + \frac{k_4}{s+5 \cdot 10^3}$$


Natural poles Forced poles

- $k_1 = -65/6$
- $k_2 = 40/3$
- $k_3 = 20$
- $k_4 = -45/2$

$$V_2(t) = \left[\underbrace{\frac{-65}{6} e^{-1000t} + \frac{40}{3} e^{-4000t}}_{\text{Natural response}} + \underbrace{20 - \frac{45}{2} e^{-5000t}}_{\text{Forced response}} \right] u(t)$$

steady-state resp. \uparrow


Test Signals

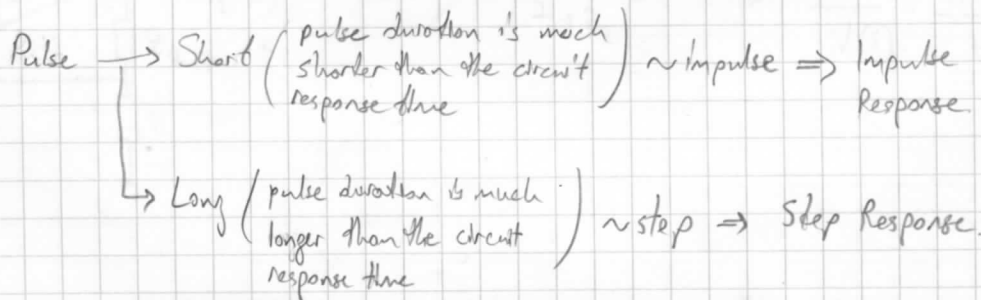

Sinusoid \rightarrow Sinusoidal Steady-State \Rightarrow Freq. Resp.

(How circuit responds to signals with varying freq)

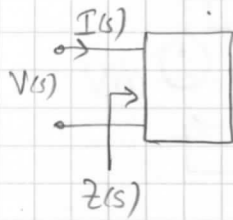11.2 Network Functions of One-Port & 2-port circuits





Driving Point Impedance

$$Z(s) = \frac{V(s)}{I(s)}$$

• Driving point impedance s-domain generalization of input resistance

• Inverse is also a Network Function

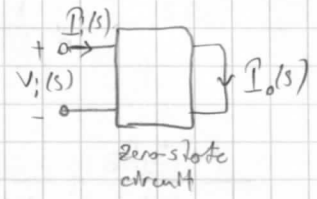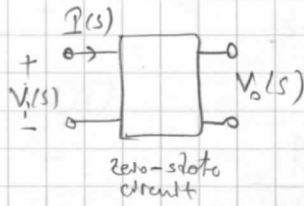


Transfer Function

$$\frac{V_0(s)}{V_1(s)} = T_V(s)$$

$$\frac{V_0(s)}{I_1(s)} = T_2(s)$$

$$\frac{I_0(s)}{I_1(s)} = T_I(s)$$

$$\frac{I_0(s)}{V_1(s)} = T_Y(s)$$

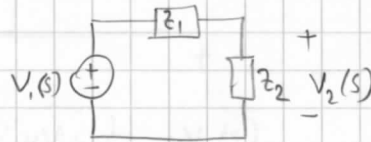


$$V_2(s) = \frac{Z_2}{Z_1 + Z_2} V_1$$

$$T_V(s) = \frac{Z_2}{Z_1 + Z_2}$$

• Inverse is not a network function

example

Inverting amplifier

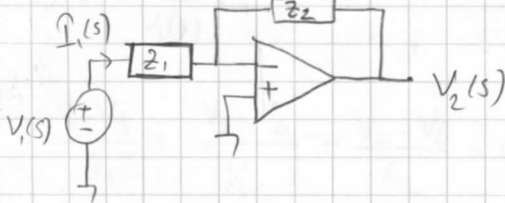


$$V_2(s) = -\frac{Z_2}{Z_1} V_1(s)$$

$$T_V(s) = -Z_2/Z_1$$

Driving point Impedance


$$\frac{V_1(s)}{I_1(s)} = Z_1$$

Non-inverting amplifier

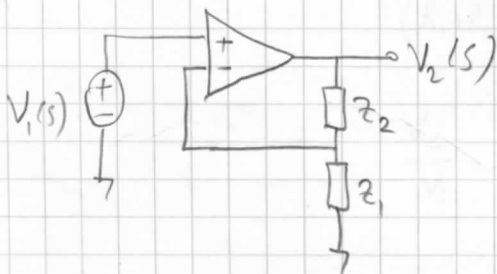

$$V_1(s) = \frac{Z_1}{Z_1 + Z_2} V_2(s) \Rightarrow \frac{V_2(s)}{V_1(s)} = \frac{Z_1 + Z_2}{Z_1} = T_V(s)$$

example

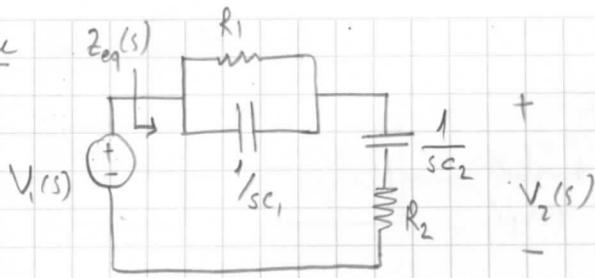

$$Z_{eq}(s) = \frac{1}{sC_1 + \frac{1}{R_1}} + R_2 + \frac{1}{sC_2}$$


$$= \frac{R_1}{sR_1C_1 + 1} + \frac{sR_2C_2 + 1}{sC_2}$$

$$= \frac{sR_1C_1 + s^2R_1R_2C_1C_2 + 1 + sR_1C_1 + sR_2C_2}{sC_2(1 + sR_1C_1)}$$

Transfer function

$$T_V(s) = \frac{\frac{sR_2C_2 + 1}{sC_2}}{\frac{R_1}{1 + sR_1C_1} + \frac{sR_2C_2 + 1}{sC_2}}$$

example

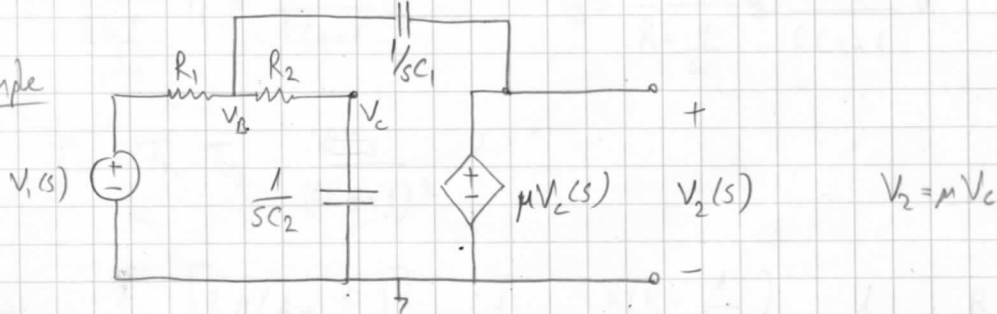

$$T_V(s) = \frac{V_2(s)}{V_1(s)} = ?$$

Node B

$$\frac{V_1 - V_B}{R_1} + \frac{V_2 - V_B}{\frac{1}{sC_1}} + \frac{V_C - V_B}{R_2} = 0$$

$$\begin{bmatrix} -R_2 - R_1 - sR_1R_2C_1 & R_1 + \mu R_1R_2C_1s \\ -1 & sC_2R_2 + 1 \end{bmatrix} \begin{bmatrix} V_B \\ V_C \end{bmatrix} = \begin{bmatrix} -R_2V_1 \\ 0 \end{bmatrix}$$

Node C


$$\frac{V_C}{\frac{1}{sC_2}} + \frac{V_C - V_B}{R_2} = 0$$

$$(R_1 + R_2 + sR_1R_2C_1)(sR_2C_2 + 1)V_C - (R_1 + s\mu R_1R_2C_1)V_C = R_2V_1$$

$$\frac{V_C}{V_1} = \frac{R_2}{(R_1 + R_2 + sR_1R_2C_1)(sR_2C_2 + 1) - (R_1 + s\mu R_1R_2C_1)}$$


$$T_V(s) = \mu \frac{V_C}{V_1}$$

Cascade Connection

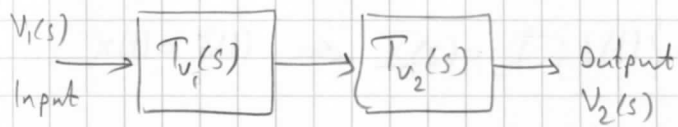

$$\frac{V_2(s)}{V_1(s)} = T_{v1}(s) T_{v2}(s) ??$$

{ True if there is no loading }

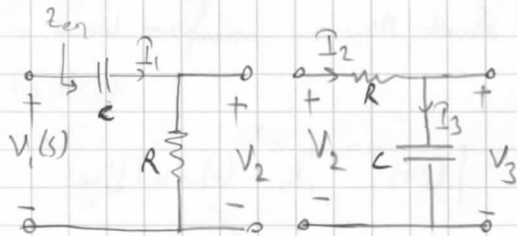

$$V_2 = \frac{R}{R + \frac{1}{sC}} V_1 = \frac{RCs}{RCs + 1} V_1 ; \quad V_3 = \frac{1/sC}{R + \frac{1}{sC}} V_2 = \frac{1}{RCs + 1} V_2$$

$$T_v = T_{v1} T_{v2} = \frac{RCs}{(RCs + 1)^2} ?$$

$$Z_{eq} = \frac{1}{sC} + \left[R \parallel \left(R + \frac{1}{sC} \right) \right] = \frac{1}{sC} + \frac{R \left(R + \frac{1}{sC} \right)}{2R + \frac{1}{sC}} = \frac{1}{sC} + \frac{R(1 + sRC)}{1 + 2sRC}$$

$$= \frac{s^2 R^2 C^2 + 3sRC + 1}{sC(1 + 2sRC)}$$


$$I_1 = \frac{V_1}{Z_{eq}} , \quad I_3 = \frac{R}{2R + \frac{1}{sC}} \frac{V_1}{Z_{eq}} = \frac{sRC}{1 + 2sRC} \frac{V_1}{Z_{eq}}$$

$$V_3 = \frac{1}{sC} I_3 = \frac{R}{1 + 2sRC} \cdot \frac{sC(1 + 2sRC)}{s^2 R^2 C^2 + 3sRC + 1} V_1$$

$$T_v = \frac{sRC}{(sRC)^2 + 3sRC + 1} \neq \frac{sRC}{(sRC + 1)^2} = T_{v1}(s) T_{v2}(s)$$

The second circuit loads the first circuit.

this method works for such circuits.

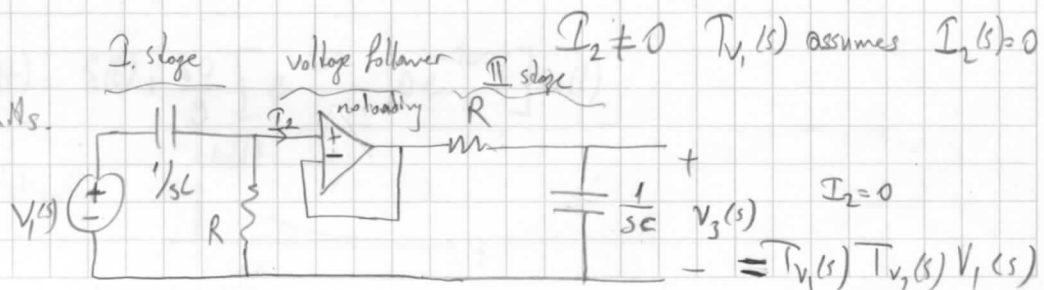

11.3 Network Functions and Impulse Response

$$x(t) = \delta(t) \Rightarrow \bar{X}(s) = \mathcal{L}\{\delta(t)\} = 1 \text{ then } Y(s) = T(s)\bar{X}(s) = T(s)$$

To avoid confusion we will denote impulse response transform as $H(s)$

{ Impulse response Transform }

$$y(t) = h(t) = \mathcal{L}^{-1}\{H(s)\}$$

↓
Impulse response


$$H(s) = \frac{k_1}{s-p_1} + \frac{k_2}{s-p_2} + \dots + \frac{k_N}{s-p_N}$$

Natural Poles

$$h(t) = (k_1 e^{p_1 t} + k_2 e^{p_2 t} + \dots + k_N e^{p_N t}) u(t)$$

For any input: $Y(s) = H(s)\bar{X}(s) \rightarrow y(t) = \mathcal{L}^{-1}\{H(s)\bar{X}(s)\}$

example

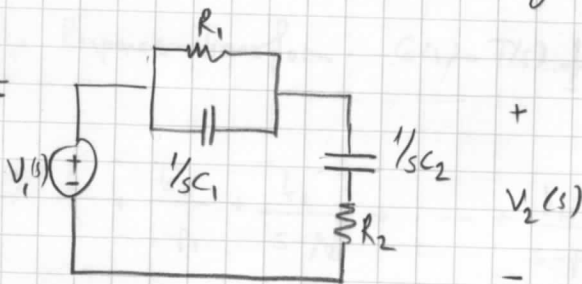

$$\frac{V_2(s)}{V_1(s)} = T_V(s) = \frac{(s + \frac{1}{R_1 C_1})(s + \frac{1}{R_2 C_2})}{s^2 + (\frac{1}{R_2 C_2} + \frac{1}{R_1 C_1} + \frac{1}{R_2 C_1})s + \frac{1}{R_1 C_1 R_2 C_2}}$$


let $R_1 = 10k\Omega$ $C_1 = 1\mu F$
 $R_2 = 12.5k\Omega$ $C_2 = 2\mu F$

$$T_V(s) = \frac{(s+100)(s+40)}{s^2 + (40+100+80)s + 4000} = \frac{(s+100)(s+40)}{(s+20)(s+200)} \Rightarrow H(s) = 1 + \frac{80/9}{s+20} - \frac{800/9}{s+200}$$

Impulse Response:

$$h(t) = \delta(t) + \frac{80}{9} [e^{-20t} - 10e^{-200t}] u(t)$$

↓
asymptotically stable

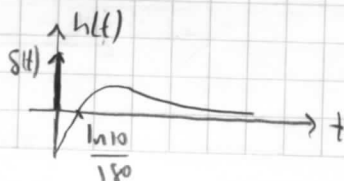


For a step input

$$V_2(s) = T_v(s) \frac{1}{s} = \frac{1}{s} + \frac{80/9}{s(s+20)} - \frac{800/9}{s(s+200)} = \frac{1}{s} + \frac{A}{s} + \frac{B}{s+20} + \frac{C}{s} + \frac{D}{s+200}$$

$$A = \frac{4}{9}, B = -\frac{4}{9}, C = -\frac{4}{9}, D = \frac{4}{9}$$
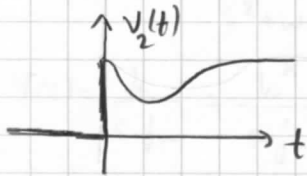
$$V_2(s) = \frac{1}{s} - \frac{4/9}{s+20} + \frac{4/9}{s+200} \Rightarrow v_2(t) = u(t) - \frac{4}{9} e^{-20t} u(t) + \frac{4}{9} e^{-200t} u(t)$$



Step Response

zero-state response of the circuit output when the input is unit step.

Step Response Transform $G(s) = T(s) \frac{1}{s}$; step response waveform $g(t) = \mathcal{L}^{-1} \left\{ \frac{T(s)}{s} \right\}$

$$G(s) = \frac{k_0}{s} + \frac{k_1}{s-p_1} + \frac{k_2}{s-p_2} + \dots + \frac{k_N}{s-p_N}$$

Forced pole

Natural Poles

$$g(t) = k_0 u(t) + \left(\sum_{i=1}^N k_i e^{p_i t} \right) u(t)$$

When the circuit is stable \Rightarrow natural response decay to zero

and


k_0 : DC steady-state response

$$G(s) = \frac{T(s)}{s} \Rightarrow g(t) = \int_0^t h(\tau) d\tau$$

$$k_0 = \lim_{s \rightarrow 0} s G(s) = T(0)$$

$$\frac{dg(t)}{dt} = h(t)$$

almost everywhere

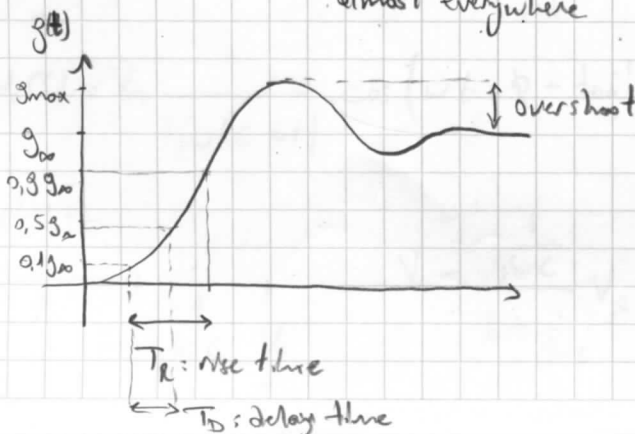

11.5 Network Functions and Sinusoidal Steady-State Response

$$x(t) = X_A \cos(\omega t + \phi)$$

$$x(t) = X_A (\cos \omega t \cos \phi - \sin \omega t \sin \phi)$$

$$X(s) = X_A \left[\cos \phi \frac{s}{s^2 + \omega^2} - \sin \phi \frac{\omega}{s^2 + \omega^2} \right] = X_A \frac{s \cos \phi - \omega \sin \phi}{s^2 + \omega^2}$$

$$Y(s) = X_A \frac{s \cos \phi - \omega \sin \phi}{s^2 + \omega^2} T(s)$$

$$Y(s) = \underbrace{\frac{k}{s-j\omega} + \frac{k^*}{s+j\omega}}_{\text{forced poles}} + \underbrace{\sum_i \frac{k_i}{s-p_i}}_{\text{Natural resp.}}$$

- If the circuit is stable, natural resp. decays to zero

$$y_{ss}(t) = k e^{j\omega t} + k^* e^{-j\omega t} : \text{steady-state response}$$

$$k = (s-j\omega) X_A \frac{s \cos \phi - \omega \sin \phi}{s^2 + \omega^2} T(s) \Big|_{s=j\omega}$$

$$y_{ss}(t) = |T(j\omega)| X_A \cos(\omega t + \phi + \theta)$$


$$\text{where } \theta = \angle T(j\omega)$$

$$\text{Amplitude} = X_A |T(j\omega)|$$

$$\text{Phase} : \text{Input Phase} + \angle T(j\omega)$$

$$= X_A \frac{j\omega \cos \phi - \omega \sin \phi}{j2\omega} T(j\omega)$$
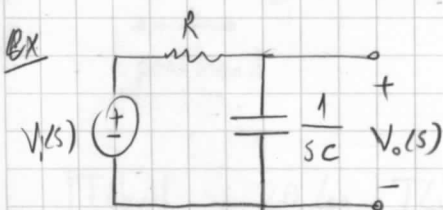
$$= X_A \frac{\cos \phi + j \sin \phi}{2} T(j\omega) = \frac{1}{2} X_A e^{j\phi} T(j\omega)$$



$$T(s) = \frac{\frac{1}{sC}}{\frac{1}{sC} + R} = \frac{1}{sRC + 1}$$

$$v_1(t) = V_A \cos(\omega t + \phi)$$

$$V_0(s) = V_A \frac{1}{j\omega RC + 1} \cos(\omega t + \phi - \tan^{-1}(RC\omega))$$

using phasors



$$V_0 = \frac{1}{R + \frac{1}{j\omega C}} V_A \angle \phi = \frac{V_A}{j\omega RC + 1} \angle \phi = \frac{V_A}{|j\omega RC + 1|} \angle \phi - \tan^{-1}(RC\omega)$$