

EE201 LABORATORY

EXPERIMENT DESIGN ASSIGNMENT-1

Design a 4 bit Analog to Digital Converter (ADC) using Op-Amps.

- Theoretical background and mathematical clarification of the assignment,
- Determine your component values,
- DC measurement and required explanations,
- Comment on your results.