

EE201 LABORATORY

EXPERIMENT DESIGN ASSIGNMENT-3

Design an average calculator using a single Op-Amp.

- Theoretical background and mathematical clarification of the assignment,
- Determine your component values,
- DC measurement and required explanations,
- Comment on your results.