

## EXPERIMENT #4

### RC COUPLED TRANSISTOR AMPLIFIER

Small signal transistor stages can be coupled by use of resistive-capacitive (RC) type networks. The use of coupling and bypass capacitors cause the transfer gain of the amplifier to fall-off at low frequencies. Amplifiers not employing coupling and bypass capacitors such as DC amplifiers are capable of amplifying very low frequency signals. The capacitor  $C_1$  in Figure 4-1 couples the AC signal source to the active device and blocks the DC components.

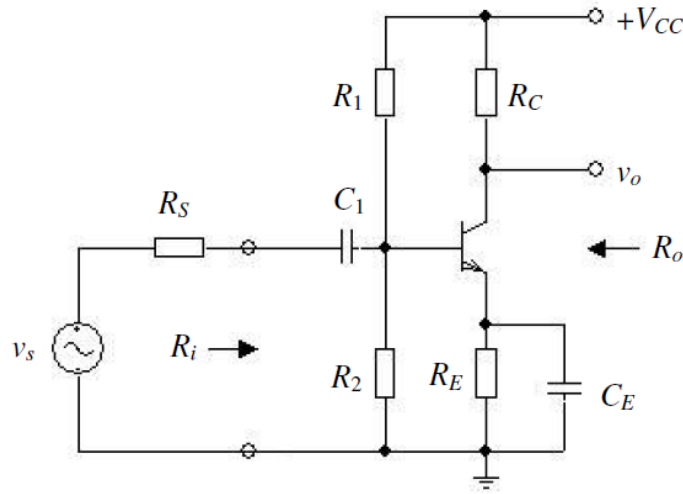


Figure 4-1: Single Stage RC-Coupled, Common Emitter Transistor Amplifier

The voltage gain for the transistor circuit with input coupling is:

$$A_v(s) = \frac{-h_{fe} R_B R_C}{[R_S (R_B + h_{ie}) + R_B h_{ie}]} \cdot \frac{s}{s + \frac{1}{C_1 [R_S + (R_B // h_{ie})]}}$$

which can be written as:

$$A_v(s) = -\frac{R_C}{r_e} \cdot \frac{R_i}{R_S + R_i} \cdot \frac{s}{s + \frac{1}{C_1 (R_S + R_i)}}$$

where

$$r_e = \frac{h_{ie}}{h_{fe}} = \frac{0.026}{I_E}, \quad R_i = R_B // h_{ie} \quad \text{and} \quad R_B = R_1 // R_2$$

The pole frequency of this transfer function is:

$$f_p = \frac{1}{2\pi C_1 (R_S + R_i)}$$

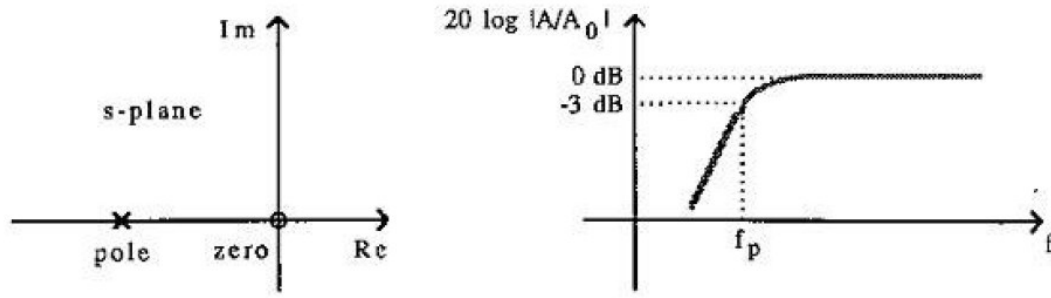


Figure 4-2: The pole-zero diagram and Bode plot of gain (the effect of coupling capacitor)

In the midband range,  $C_1$  can be assumed short circuit, hence

$$A_o = A_v(\text{midband}) = -\frac{R_C}{r_e} \cdot \frac{R_i}{R_S + R_i}$$

$$A_o \approx -\frac{R_C}{r_e} \quad \text{if } R_S \ll R_i$$

The pole-zero diagram and asymptotic Bode plot of gain are shown in *Figure 4-2*. The effect of adding an emitter resistor  $R_E$  with bypass capacitor  $C_E$  produces essentially the same effect as the input and output coupling capacitors. The voltage gain can be written as:

$$A_v(s) = \frac{-h_{fe} R_B R_C}{[R_B R_S + h_{ie} R_B + h_{ie} R_S]} \cdot \frac{s + \frac{1}{R_E C_E}}{s + \frac{1}{R_E C_E} + \frac{1 + h_{fe}}{C_E [h_{ie} + (R_B \parallel R_S)]}}$$

this can be rearranged for  $h_{fe} \gg 1$ :

$$A_v(s) = -\frac{R_C}{r_e} \cdot \frac{R_i}{R_S + R_i} \cdot \frac{s + \frac{1}{R_E C_E}}{s + \frac{1}{R_E \parallel [r_e + (R_S \parallel R_B) / h_{fe}] C_E}}$$

The zero and pole frequencies are respectively:

$$f_0 = \frac{1}{2\pi R_E C_E}$$

$$f_p = \frac{1}{2\pi \left\{ R_E \parallel \left[ r_e + \frac{R_S \parallel R_B}{h_{fe}} \right] \right\} C_E}$$

In most cases:

$$(R_S // R_B) / h_{fe} \ll r_e \ll R_E$$

and

$$f_p \approx \frac{1}{2\pi r_e C_E}$$

In the midband frequency range, the emitter capacitor can be assumed short circuit and the gain can be found as:

$$A_o \approx -\frac{R_C}{r_e} \quad \text{if } R_S \ll R_i$$

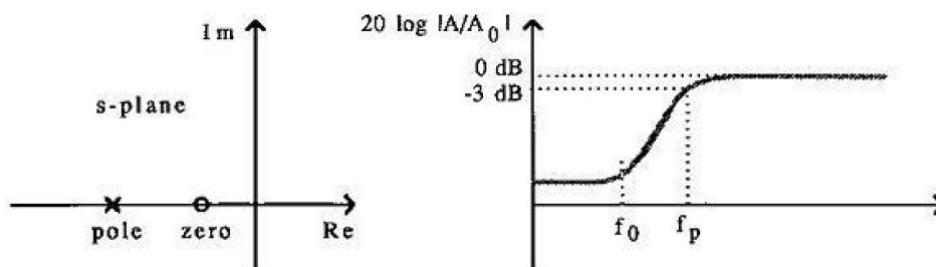


Figure 4-3: The pole-zero diagram and Bode plot of gain (the effect of Emitter bypass capacitor)

In most applications, both  $C_E$  and  $C_1$  are present and the analysis is very complicated. However, the emitter bypass capacitor usually determines the low-frequency response, and this requires that the pole frequency due to  $C_1$  be far below the pole frequency due to  $C_E$ . This implies that:

$$\frac{1}{C_1(R_S + R_i)} \ll \frac{1}{C_E r_e}$$

For most cases  $r_e < (R_S + R_i)$ , but this situation may change when one chooses  $C_E \gg C_1$ . The amplifier input and output impedances are also frequency dependent. However, these are normally specified for the midband frequency range. For the common emitter amplifier:

$$R_i = R_B // h_{ie} \approx h_{ie} = h_{fe} r_e$$

$$R_o = R_C // (1/h_{oe}) \approx R_C$$

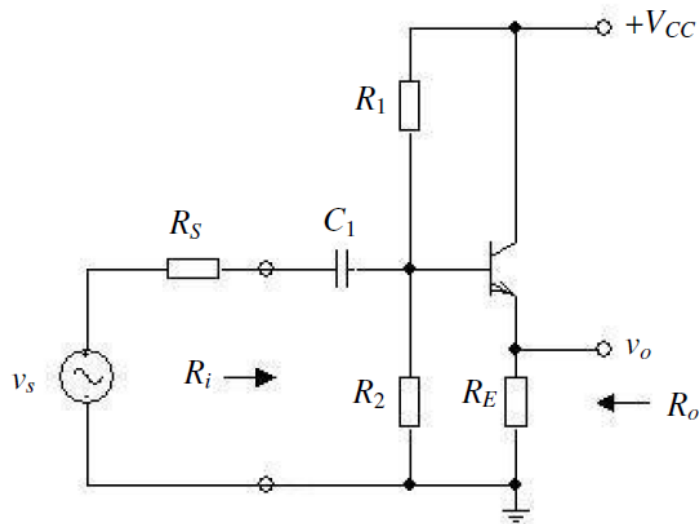


Figure 4-4: Emitter Follower Circuit

and for the emitter follower circuit:

$$R_i = R_B \parallel [h_{fe}(r_e + R_E)] \approx R_B \parallel (h_{fe} R_E)$$

$$R_o = R_E \parallel \left[ r_e + \frac{R_S \parallel R_B}{h_{fe}} \right] \approx r_e$$

## EQUIPMENT

1. CRT oscilloscope
2. Audio signal generator
3. Electronic A.C. voltmeter
4. Decade resistor box
5. Bread-board

## COMPONENTS

1. Transistor: BC238B or equivalent
2. Capacitors: 100 nF, 1 $\mu$ F, 10 $\mu$ F and 100 $\mu$ F
3. Resistors: 270k, 82k, 2k7, 1k

## PROCEDURE

1. Set-up the circuit shown in *Figure 4-5*. Calculate the D.C. operating point and  $A_v$ ,  $R_i$ ,  $R_o$  for both emitter follower and common emitter configuration.

Calculated :  $V_{CEQ} = \dots\dots\dots$                        $I_{CQ} = \dots\dots\dots$

Measured :  $V_{CEQ} = \dots\dots\dots$                        $I_{CQ} = \dots\dots\dots$

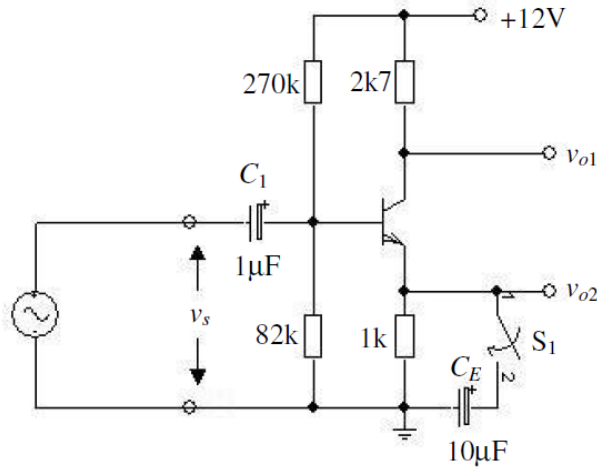


Figure 4-5: Experimental Single Stage Amplifier


2. Apply a 20mVpp-10kHz sine wave to the input and measure  $v_{o1}$  (when S1 is closed) and  $v_{o2}$  (when S1 is opened). Calculate the voltage and the current gains of common emitter amplifier and emitter follower circuits respectively.

$v_{o1} = \dots\dots\dots$                        $v_{o2} = \dots\dots\dots$

$A_{v1} = \dots\dots\dots$                        $A_{v2} = \dots\dots\dots$                        $A_{i1} = \dots\dots\dots$                        $A_{i2} = \dots\dots\dots$

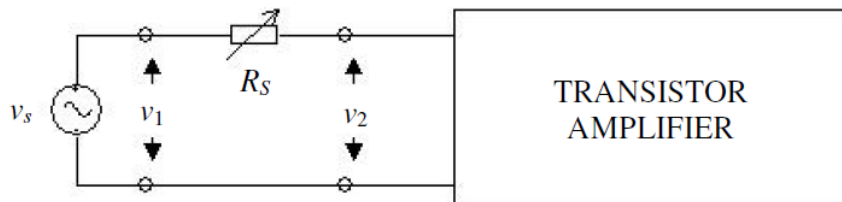3. Insert a resistor decade box between the source and the input. Adjust  $R_S$  to obtain  $v_2 = v_1 / 2$ . The input impedance is then equal to  $R_S$ .

$R_i$  (common emitter) =  $\dots\dots\dots$



4. Open the switch S1 and repeat step 3 for the emitter follower circuit.

$R_i$  (emitter follower) =  $\dots\dots\dots$

5. Apply the following procedure to measure the collector and the emitter output impedances:

Measure the amplitude of the A.C. signal  $v_1$  with the switch  $S_2$  open. Now close the switch and adjust  $R_L$  until  $v_1$  is halved. The output impedance  $R_o$  is then equal to  $R_L$ .

$R_o$  (collector)= .....



6. Repeat step 5 for the emitter follower circuit.

$R_o$  (emitter)= .....

7. Using the set-up in *Figure 4-5* apply a 10kHz sine wave to the amplifier and adjust  $v_{in}$  until you see a distortionless output waveform. Take the peak value of this signal as your reference voltage  $v_r$ . Then keeping the input voltage constant, change the frequency and read the output voltage  $v_o$ . Take enough data to make a rough plot of the voltage gain as the input frequency is varied. Measure the lower 3dB frequency and compare with your calculated value.

$f$ (Hz)	100	200	500	1000	2000	5000	10000
$20 \log (v_o / v_r)$ (dB)							0

$f(-3dB) = \dots\dots\dots$

8. Sketch and dimension the Bode magnitude plots of the voltage gains on semi-log paper.

