

EE 311 LT-SPICE HW#1

Q-1) Consider the following circuit as illustrated in Fig.1. Apply a sinusoidal voltage supply to the input with $20V_{p-p}$ and 50Hz. Select time domain analysis for 100ms.

- Construct this circuit in LT-SPICE for “Ideal Diode” model with zero on resistance. Plot input voltage, diode current and output voltages.
- For ideal diode model in a), calculate ripple voltage value (V_r) and maximum diode current (i_{Dmax}).
- Construct this circuit with “diode.txt” of CMOS Spice Lib Files at the website.
- Repeat calculations in b) for construction in step of c) with “diode.txt” model.
- Compare results of ideal model and “diode.txt” and explain differences.

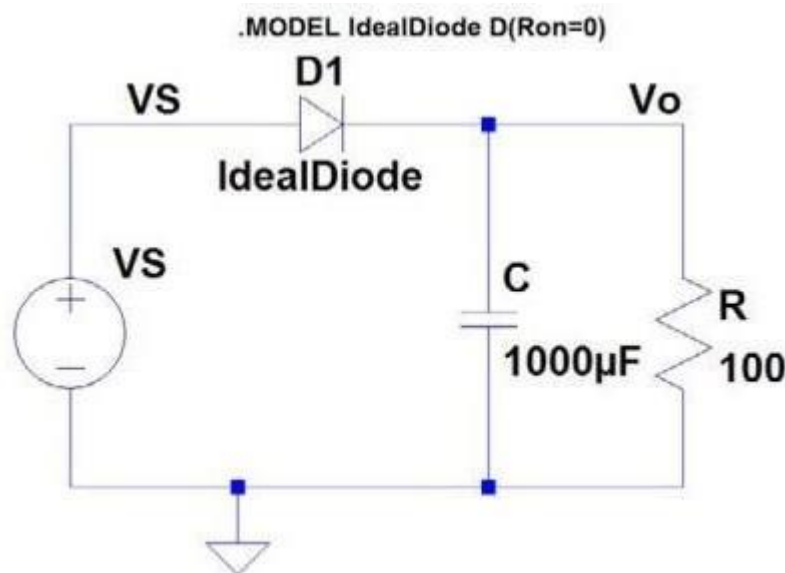


Fig.1: Half Wave Rectifier With a Smoothing Filter

Q-2) Consider the Fig.2.

- In this circuit, calculate τ comes from capacitor and resistors.
- Calculate capacitor voltage at the time of τ .
- Construct the circuit in LT-SPICE with PWL source for transient simulation of 8ms as depicted in Fig.2. In here, PWL source should start with zero value. After that, it has a pretty good rising time as a 2us and it goes up to the 6V. It stays at 6V for a 3ms. Then it decreases all of a sudden with falling time of 0.2us. It is ended up with zero volt. In this respect, check the capacitor voltage that you calculated in b). **Hint:** Utilize from cursor attachment. Show the results. Comment on the differences between your calculation and SPICE's result.

 


Fig.2: A RC network with PWL source

NOTE: Please, show all your calculations step by step for partially credit.