

*Objectives: In this experiment, simple op-amp circuit, inverting, summing and difference amplifiers, will be investigated and analyzed.*

*Materials:*

Breadboard  
DMM (Digital multi-meter)  
Signal Generator(s)  
DC Power Supply  
Oscilloscope  
Resistor(s)  
LM741

*Procedure:*

1. A (-n inverting) summation amplifier having three inputs is to be designed. Gains of these inputs will be 3,2,1 respectively.

Input 1: A sinusoidal signal having a peak to peak amplitude of 1 [V], and a frequency of 20 [kHz].

Input 2: A triangular wave having a peak to peak amplitude of 4 [V], and a frequency of 2 [kHz].

Input 3: A dc signal having an amplitude of -1 [V].

- a) Determine resistor values (use: 10k, 5.6k, 3.3k, 2.2k)
- b) Determine op-amp feeding voltages with respect to your amplification gains.
- c) Guess and sketch output signal.
- d) Construct the circuit, record input and output voltages.
- e) Show frequency and amplitude contributions of each input component at the output waveform.

2. A difference amplifier is to be constructed. Gain is desired to be two times of the input.

Input: a sinusoidal signal having peak to peak amplitude of 3 [V], and frequency of 10 [kHz].

- a) Determine resistor values (use: 10k, 5.6k, 3.3k, 2.2k)
- b) Determine op-amp feeding voltages with respect to your amplification gains.
- c) Guess and sketch output of common mode signal.
- d) Guess and sketch output of differential mode signal.
- e) Construct the circuit, record input and output voltages.