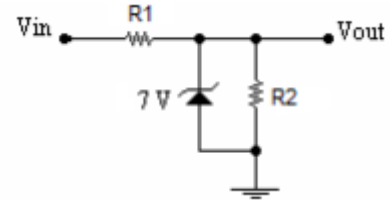


5) Consider the voltage regulator circuit for keeping $V_{out}=7\text{ V}$. The zener diode has the maximum power of $P_{ZM}=0.5\text{ W}$.

- What must be the range of the load resistor R_2 , if $R_1=100\ \Omega$ and $V_{in}=10\text{ V}$?
- What must be the range of the load resistor R_2 , if $R_1=30\ \Omega$ and $V_{in}=10\text{ V}$?
- Carefully calculate and show all valid R_1 - R_2 region in detail assuming $V_{in}=10\text{ V}$. (Use the horizontal axis R_1 for the values $R_1>0$, and the vertical axis R_2 for $R_2>0$ in a two dimensional plot. The region and the bordering functions must be clearly indicated in detail.)

Answer:

We need: $I_z>0$, and for this we need $R_2/(R_1+R_2)*V_{in}>V_z$
and we need $I_z*V_z<P_{ZM}$ where $I_z=(V_{in}-V_z)/R_1-V_z/R_2$



a)

$$R_2/(100+R_2)*10>7$$

$$10*R_2>700+7*R_2$$

$$R_2>233\text{ Ohms}$$

$$I_z=(10-7)/100-7/R_2$$

$$I_{zMAX}=30\text{mA} \rightarrow P_{ZMAX}=30\text{mA}*7=210\text{mW. This is already less than } P_{ZM} \text{ even if } R_2 \text{ is infinity.}$$

b)

$$R_2/(30+R_2)*10>7$$

$$10*R_2>210+7*R_2$$

$$R_2>70\text{ Ohms}$$

$$I_z=(10-7)/30-7/R_2$$

$$I_z=100\text{mA}-7/R_2$$

$$(100\text{mA}-7/R_2)*7<0.5$$

$$0.7-49/R_2<0.5$$

$$0.2<49/R_2$$

$$R_2<245$$

Therefore we need: $70<R_2<245$

c)

Lower Limit for R_2 given R_1 :

$$R_2/(R_1+R_2)*10>7 \rightarrow R_2>2.33*R_1$$

Upper Limit for R_2 given R_1 :

$$((10-7)/R_1-7/R_2)*7<0.5 \rightarrow 3/R_1 < 0.5/7 + 7/R_2$$

$$\rightarrow 7/R_2 > 3/R_1 - 0.5/7$$

Therefore, if $3/R_1<0.5/7$, or, $R_1>42$ there is no upper limit for R_2 .

When $R_1<42$ we need:

$$R_2<98*R_1/(42-R_1)$$

