
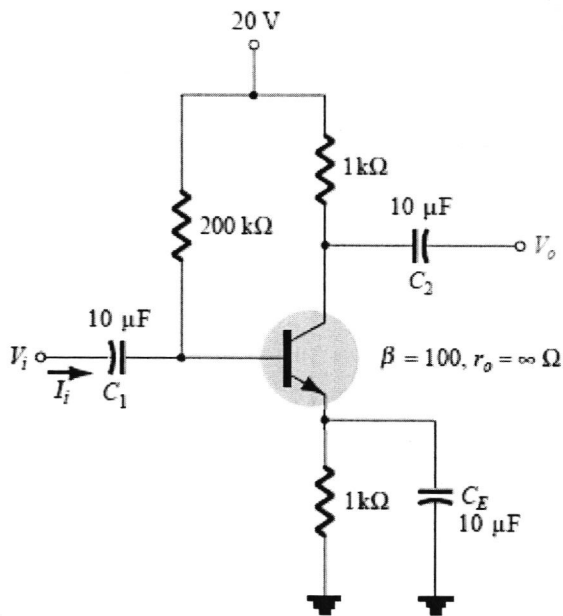


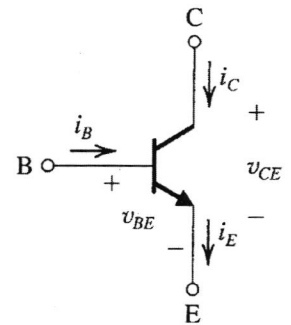1) For the network, find the DC currents I_B , I_E , and the DC voltage V_{CE} .



Hint: npn transistor equations in active mode are:

$$i_C = \beta i_B \quad v_{BE} = 0.7$$



$$20 = 200\text{K} \cdot I_B + 0.7 + 1\text{K} \cdot \underbrace{101 \cdot I_B}_{I_E}$$




$$\Rightarrow I_B = 0.064 \text{ mA}$$

$$\Rightarrow I_E = 6.48 \text{ mA}$$

$$20 = 1\text{K} \cdot \underbrace{100 \cdot I_B}_{I_C} + V_{CE} + 1\text{K} \cdot I_E$$


$$\Rightarrow V_{CE} = 7.1 \text{ V}$$

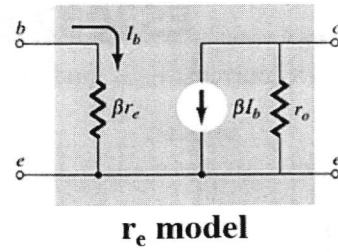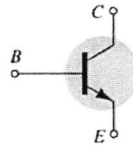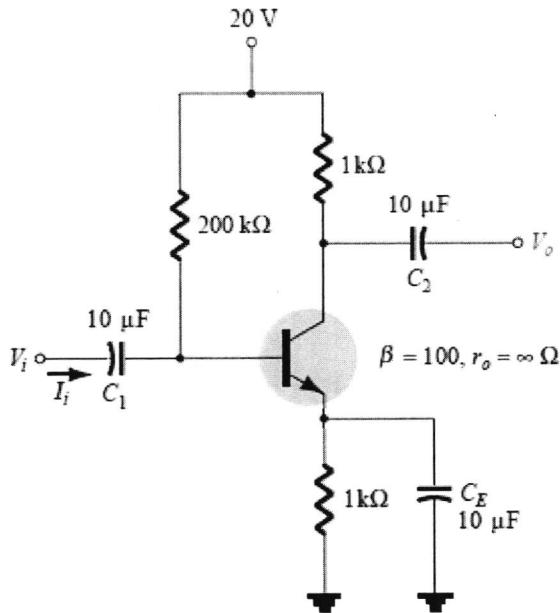2) For the network shown, assume $r_e = 4 \Omega$. Draw the ac equivalent network, and find the voltage gain V_o/V_i .



$$I_e = (\beta + 1)I_b$$

$$r_e = \frac{26 \text{ mV}}{I_e}$$

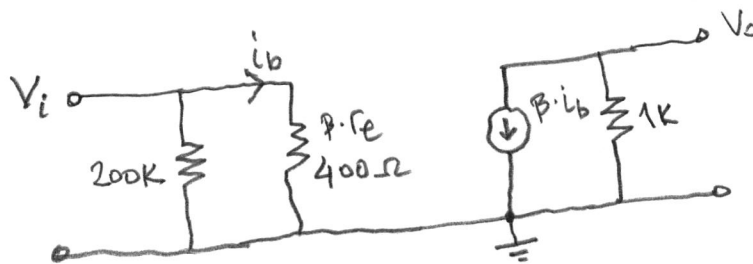


$$i_b = \frac{V_i}{\beta \cdot r_e}$$

$$V_o = -1\text{k} \cdot \beta \cdot i_b$$

$$\Rightarrow \frac{V_o}{V_i} = -\frac{1\text{k}}{r_e} = -250$$

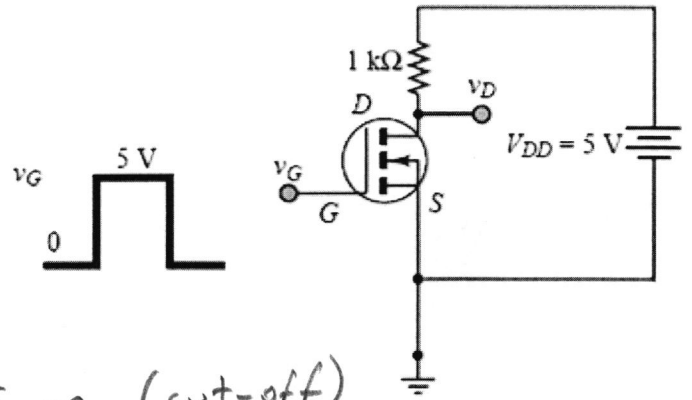3) The NMOS transistor shown in the figure has $V_{GS(Th)} = 2.5 \text{ V}$, $k = 1 \text{ mA/V}^2$. If v_G is a pulse with 0 V to 5 V, find the voltage levels of the pulse signal at the drain output. (That is; find v_D for $v_G = 0$ and for $v_G = 5 \text{ V}$)



For $V_G = V_{GS} = 0 \Rightarrow I_D = 0$ (cut-off)
 $V_D = 5 - 1k \cdot I_D = \underline{\underline{5}}$

For $V_G = V_{GS} = 5 \text{ V}$:

Assume saturation first: $I_D = k \cdot (5 - 2.5)^2 = 6.25 \text{ mA}$

$\Rightarrow V_D = V_{DS} = 5 - 1k \cdot I_D = -1.25 \text{ V}$

which is impossible ($V_{DS} < V_{GS} - V_{GS(Th)}$)

Assume Ohmic region:

$I_D = k \cdot [2(5 - 2.5)V_D - V_D^2]$

and from the circuit $I_D = \frac{5 - V_D}{1k}$

$\Rightarrow 5 - V_D = 5V_D - V_D^2$

$\Rightarrow \underline{\underline{V_D = 1}}$ (the other root, 5, is not valid.)

$I_D = 4 \text{ mA}$

- If $V_{GS} < V_{GS(Th)}$, the NMOS is in cut-off, $I_D = 0$. Otherwise:
 - If $V_{DS} < V_{GS} - V_{GS(Th)}$, the NMOS is in Triode (Ohmic) region, in this case:

$$I_D = k[2(V_{GS} - V_{GS(Th)})V_{DS} - V_{DS}^2]$$
 - If $V_{DS} \geq V_{GS} - V_{GS(Th)}$, the NMOS is in Saturation region, in this case:


$$I_D = k(V_{GS} - V_{GS(Th)})^2$$

$I_G = 0 \text{ A}, I_D = I_S$

V_T
 $I_{D(on)}$
 $V_{GS(on)}$

$I_D = k(V_{GS} - V_{GS(Th)})^2$
 $k = \frac{I_{D(on)}}{(V_{GS(on)} - V_{GS(Th)})^2}$

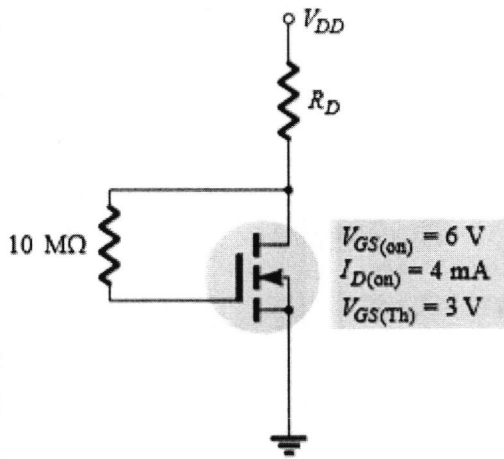4) For the network shown, we need $V_{DS} = V_{DD}/2$, and $I_D = 1 \text{ mA}$. Determine V_{DD} and R_D .



$$k = \frac{4 \text{ mA}}{(6-3)^2} = \frac{4}{9} \text{ mA/V}^2$$

Since $V_{DS} = V_{GS}$, NMOS is in saturation.

$$I_D = k \cdot (V_{GS} - V_{GS(Th)})^2$$

$$1 = \frac{4}{9} (V_{GS} - 3)^2$$

$$\Rightarrow V_{GS} = V_{DS} = 4.5 \text{ V.}$$

$$\Rightarrow V_{DD} = 2 \cdot 4.5 = \underline{\underline{9 \text{ V.}}}$$

$$R_D = \frac{V_{DD} - V_{DS}}{I_D} = \frac{9 - 4.5}{1} = \underline{\underline{4.5 \text{ k}\Omega}}$$

- If $V_{GS} < V_{GS(Th)}$, the NMOS is in cut-off, $I_D = 0$.
Otherwise:

- If $V_{DS} < V_{GS} - V_{GS(Th)}$, the NMOS is in Triode (Ohmic) region, in this case:

$$I_D = k[2(V_{GS} - V_{GS(Th)})V_{DS} - V_{DS}^2]$$

- If $V_{DS} \geq V_{GS} - V_{GS(Th)}$, the NMOS is in Saturation region, in this case:

$$I_D = k(V_{GS} - V_{GS(Th)})^2$$

