
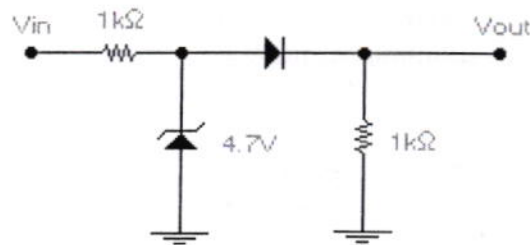


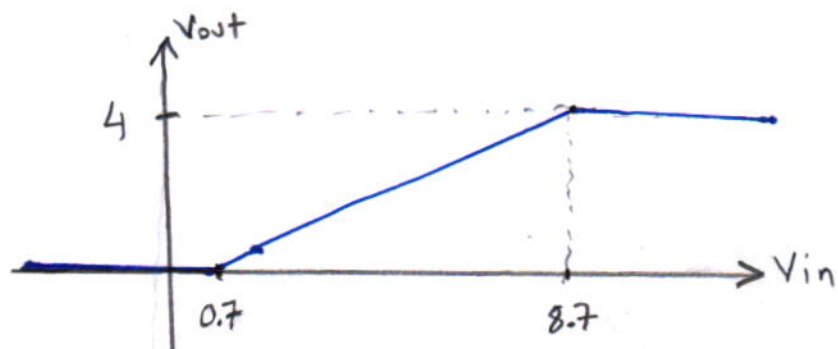
1) For the circuit in the figure, assume the diode is (0.7 Volt) ideal. Obtain and draw input-output voltage relationship.



- if  $V_{in} < 0.7$ , the diode is off  $\Rightarrow V_{out} = 0$ .
- if  $V_{in} > 0.7$ , the diode is on:
  - if the zener off,  $I_d = \frac{V_{in} - 0.7}{2k}$ ,  $V_{out} = \frac{V_{in} - 0.7}{2}$   
 the voltage on the zener:  $\frac{V_{in} + 0.7}{2}$
  - if  $V_{in} > 8.7$ , the zener is on,  $V_{out} = 4$



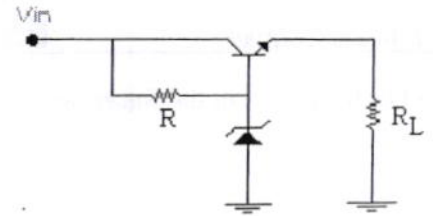2) The voltage regulator circuit given has to produce 5V on  $R_L$ . The transistor has  $\beta=100$  and  $V_{be}=0.7V$  (assume working in active region).  $R_L = 10 \Omega$ .



- What is the suitable  $V_Z$  value?
- If  $V_{in}=10V$  what should be the maximum value of  $R$ ?
- If  $R=100\Omega$ , what should be the minimum value  $V_{in}$ ?

a)  $V_Z = 5 + 0.7 = \underline{\underline{5.7 V}}$

b)  $I_E = \frac{5}{R_L} = 0.5 A$  ,  $I_B = \frac{I_E}{\beta+1} \approx 5 mA$  ,  $I_R > I_B$


$\Rightarrow R < \frac{V_{in} - 5.7}{5 mA} = \underline{\underline{860 \Omega}}$

c)  $\frac{V_{in} - 5.7}{R} > 5 mA$  ,  $V_{in} > 5.7 + 5 mA \cdot R$  ,  $\underline{\underline{V_{in} > 6.2 V}}$



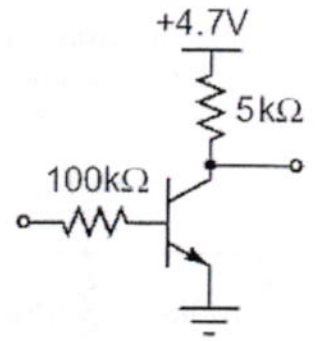3) A simple logical inverter is shown in the figure.

- When the input goes high (4.7V), the transistor should saturate as to have the minimum possible output voltage ( $V_{CEsat}=0.2$  V). What is the minimal  $\beta$  the transistor must have to saturate at an input voltage of 4.7V given the resistors as shown?
- Draw the input-output voltage transfer characteristics if the transistor has  $\beta=100$ . (Use the horizontal axis for the input voltage in the range of 0 to 4.7 volts. Use the vertical axis for the output voltage.)



$$a) \quad I_B = \frac{4.7 - 0.7}{100k} = 40 \mu A, \quad I_C = \frac{4.7 - 0.2}{5k} = 0.9 mA$$

$$\Rightarrow \beta > \frac{0.9 mA}{40 \mu A} = \underline{\underline{22.5}}$$


b) if  $V_{in} < 0.7$ , the transistor is off,  $V_{out} = 4.7$  V

if in active region:


$$I_B = \frac{V_{in} - 0.7}{100k}, \quad V_{out} = 4.7 - 5k \cdot I_B \cdot \beta$$

$$\Rightarrow V_{out} = 4.7 - 5(V_{in} - 0.7) = 8.2 - 5 \cdot V_{in}$$

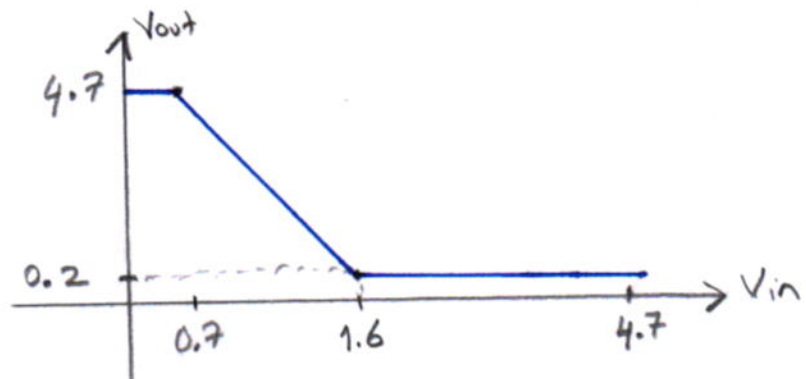if in saturation,  $V_{out} = 0.2$ ,  $V_{in} > \frac{8.2 - 0.2}{5} = 1.6$  V.



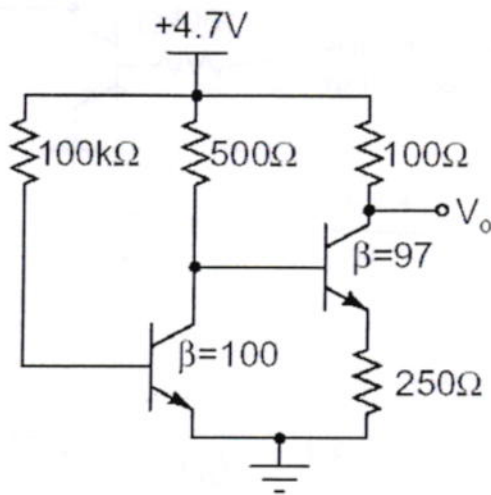4) In the transistor circuit shown below, assume that both transistors are biased in the active region. Use the index 1 for quantities pertaining to the transistor with  $\beta = 100$  and the index 2 for those pertaining to the transistor with  $\beta = 97$ . Determine  $i_{b1}$ ,  $i_{b2}$ ,  $V_{ce1}$ ,  $V_{ce2}$ , and the output voltage  $V_o$ .



$$i_{b1} = \frac{4.7 - 0.7}{100k} = 40 \mu A$$

$$i_{c1} = 4 mA$$

$$4.7 = 500 \cdot (4mA + i_{b2}) + 0.7 + 250 \cdot 98 \cdot i_{b2}$$

$$\Rightarrow i_{b2} = 80 \mu A$$

$$i_{c2} = 7.76 mA$$

$$i_{e2} = 7.84 mA$$

$$V_{ce1} = 4.7 - 500 \cdot (4mA + 80 \mu A) = \underline{\underline{2.66 V}}$$

$$V_{ce2} = 4.7 - 100 \cdot i_{c2} - 250 \cdot i_{e2} = \underline{\underline{1.96 V}}$$

$$V_o = 4.7 - 100 \cdot i_{c2} = \underline{\underline{3.92 V}}$$

