




Student Name & Number: \_\_\_\_\_

**EE2001 Final Exam**

Jan. 14, 2020

(24 pts.) 1) For each element of the circuit below, find the rms phasor voltages (V) and currents (I), together with the average powers *absorbed* (P) and the magnetizing reactive powers *absorbed* (Q). Note that the current and voltage reference directions are indicated for each element. Please fill out the table provided.

**Answer 1:**

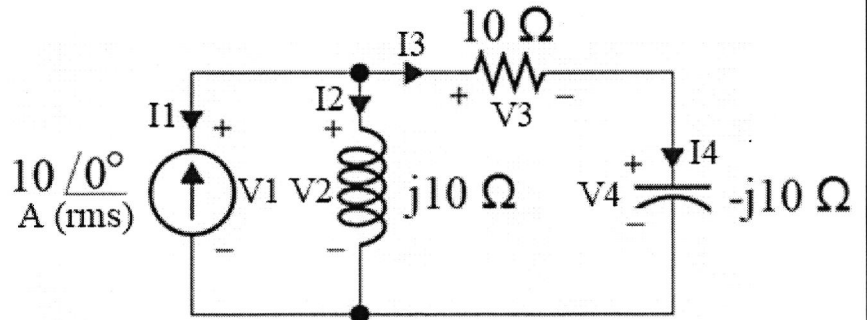

$$I_1 = -10 \text{ A}$$

$$I_2 = \frac{10 - j10}{j10 + (10 - j10)} \cdot 10 = 10 - j10 \text{ A}$$

$$I_3 = I_4 = \frac{j10}{j10 + (10 - j10)} \cdot 10 = j10 \text{ A}$$

$$V_1 = V_2 = I_2 \cdot j10 = 100 + j100 \text{ V}$$

$$V_3 = I_3 \cdot 10 = j100 \text{ V}$$

$$V_4 = I_4 \cdot (-j10) = 100 \text{ V}$$

$$S_1 = V_1 \cdot I_1^* = -1000 - j1000 \text{ VA}$$

$$S_2 = V_2 \cdot I_2^* = j2000 \text{ VA}$$

$$S_3 = V_3 \cdot I_3^* = 1000 \text{ VA}$$

$$S_4 = V_4 \cdot I_4^* = -j1000 \text{ VA}$$


Note that,  $\sum P$  and  $\sum Q$  are zero for absorbed powers.

	(1) Current Source	(2) Inductor	(3) Resistor	(4) Capacitor
V (Volts rms)	$100 \cdot \sqrt{2} \angle 45^\circ$	$100 \cdot \sqrt{2} \angle 45^\circ$	$100 \angle 90^\circ$	$100 \angle 0^\circ$
I (Amperes rms)	$10 \angle 180^\circ$	$10 \cdot \sqrt{2} \angle -45^\circ$	$10 \angle 90^\circ$	$10 \angle 90^\circ$
P (Watts)	-1000	0	1000	0
Q (VAR)	-1000	2000	0	-1000

Note: Total time allowed is 100 min. Please show all your work and write legibly.

(20 pts.) 2) Find Thevenin equivalent circuit with respect to the terminals a,b for the circuit shown.

Hint: If  $V_{TH}$  value is found to be zero, the circuit is equivalent to a pure impedance. In this case, the equivalent impedance value can be found by applying a voltage source to the terminals, and calculating the current supplied.

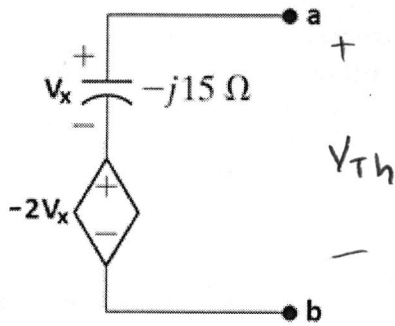

Answer 2:

Open Circuit:


$$V_{Th} = V_x - 2V_x = -V_x$$

Since the current is zero,

$$V_x = (-j15) \cdot 0 = 0$$

$$\Rightarrow V_{Th} = 0 \quad (\text{internal voltage is zero})$$

Applying a voltage source:

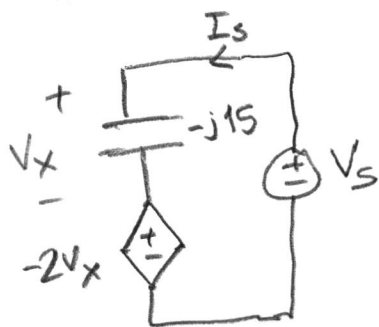


$$V_s = V_x - 2V_x = -V_x$$



$$V_x = (-j15) \cdot I_s$$

$$\Rightarrow V_s = \underbrace{(j15)}_{Z_{Th}} \cdot I_s$$

Therefore Thevenin equivalent is:

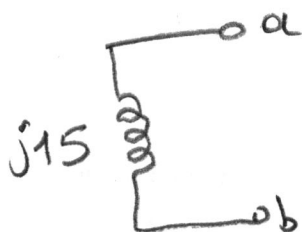

(21 pts.) 3) The switch in the circuit shown has been open for a long time. At time  $t=0$  the switch is closed. The resulting current  $i(t)$  is depicted below. Estimate the resistor and inductor values (within  $\pm 5\%$  error).

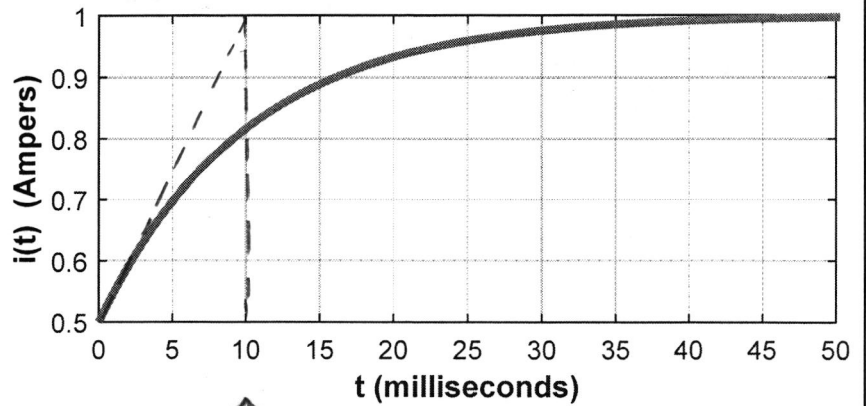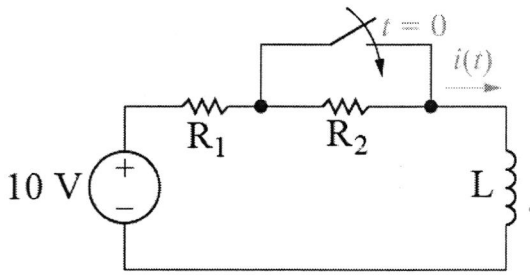

Answer 3:

Time constant  $\tau = 10 \text{ ms}$

$$\underline{t < 0} \Rightarrow i(0) = \frac{10}{R_1 + R_2} = 0.5 \text{ A}$$

$$\underline{t \rightarrow \infty} \Rightarrow i(\infty) = \frac{10}{R_1} = 1 \text{ A}$$

$$\underline{t > 0} \Rightarrow \tau = \frac{L}{R_1} = 10 \text{ ms}$$

$$\Rightarrow R_1 = 10 \Omega$$


$$R_2 = 10 \Omega$$

$$L = 100 \text{ mH}$$

(20 pts.) 4) Consider an inductive load having the voltage and the current as described below:

$$v(t) = V_m \cos(\omega t), \quad \text{and,} \quad i(t) = I_m \cos(\omega t - \theta).$$

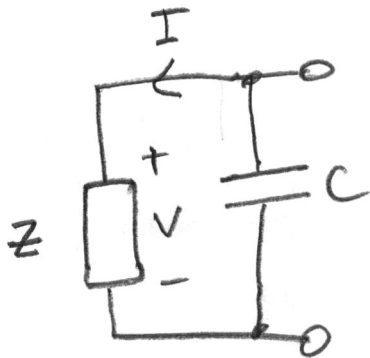Find the capacitor value  $C$  (in terms of  $V_m$ ,  $I_m$ ,  $\omega$ ,  $\theta$ ), such that, when connected in parallel with the load, will make the load look purely resistive.



$$V = V_m \angle 0^\circ$$

$$I = I_m \angle -\theta$$

$$\text{Impedance: } \Rightarrow Z = \frac{V}{I} = \frac{V_m}{I_m} \angle \theta$$

$$\text{Admittance: } Y = \frac{I_m}{V_m} \angle -\theta = \frac{I_m}{V_m} \cdot \cos(\theta) - j \frac{I_m}{V_m} \sin(\theta)$$

$$\text{Admittance of } C: Y_c = j\omega C$$


$Y + Y_c$  (in parallel) must be a real number.

$$\Rightarrow \omega C = \frac{I_m}{V_m} \cdot \sin(\theta)$$

$$\Rightarrow C = \frac{I_m}{\omega V_m} \cdot \sin(\theta)$$

(25 pts.) 5) For the circuit shown,  $v_g(t) = 0.1\sin(10^6 t)$ . Write four equations which are necessary to solve for the phasor voltages  $V_1$ ,  $V_2$ ,  $V_3$ , and  $V_4$ . Also, write an expression (in terms of the variables used) for the amount of the complex power generated by the input voltage source  $v_g$ .

**Do not** solve the equations; just write them correctly and completely.

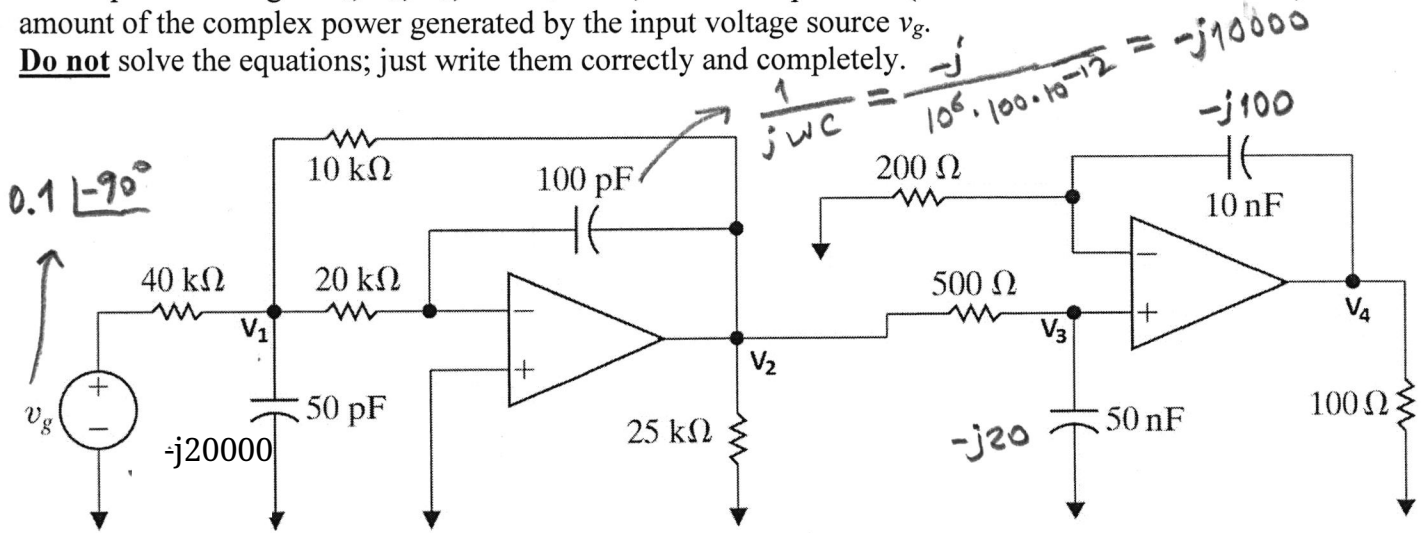

**Equation 1:**

$$\frac{V_1 + 0.1j}{40000} + \frac{V_1}{-j20000} + \frac{V_1 - V_2}{10000} + \frac{V_1 - 0}{20000} = 0$$

**Equation 2:**

$$\frac{0 - V_1}{20000} + \frac{0 - V_2}{-j10000} = 0$$

**Equation 3:**

$$\frac{V_3 - V_2}{500} + \frac{V_3}{-j20} = 0$$

**Equation 4:**

$$\frac{V_3}{200} + \frac{V_3 - V_4}{-j100} = 0$$

**An expression for the complex power generated by the source  $v_g$ :**

$$S_g = 0.5 V_g \cdot I_g^* = (-0.1j) \cdot \left( \frac{-0.1j - V_1}{40000} \right)^* \cdot 0.5$$