




Student Name: _____

EE2001 Midterm Exam

Nov. 12, 2019

(25 pts.) 1) For the circuit below, find the power delivered by the voltage source.

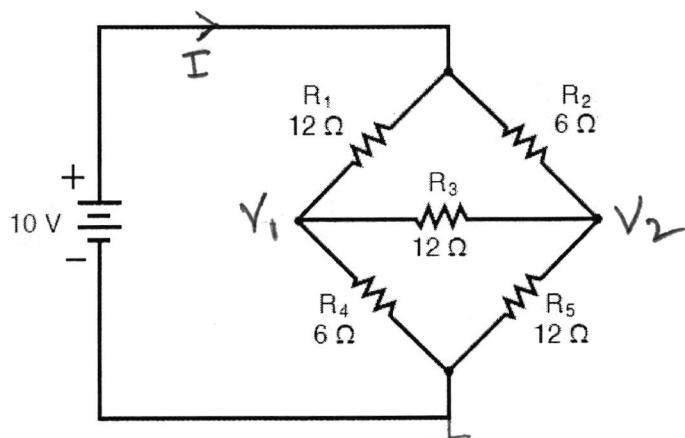

Answer 1: Using Node Voltage Analysis:

$$\frac{V_1 - 10}{12} + \frac{V_1 - V_2}{12} + \frac{V_1}{6} = 0$$

$$\frac{V_2 - 10}{6} + \frac{V_2 - V_1}{12} + \frac{V_2}{12} = 0$$

$$\Rightarrow 4V_1 - V_2 = 10 \\ -V_1 + 4V_2 = 20$$


$$\Rightarrow \underline{V_1 = 4V}, \underline{V_2 = 6V}$$

$$\Rightarrow I = \frac{10 - V_1}{12} + \frac{10 - V_2}{6} = \frac{7}{6} A$$

$$\Rightarrow \text{Power} = 10 \cdot I = \underline{\underline{\frac{35}{3} W}}$$

(25 pts.) 2) Find Thevenin equivalent for the circuit shown. (Assume, R is a known resistor value.)

Hint: If V_{TH} value is found to be zero, the circuit is equivalent to a pure resistor. In this case, the equivalent resistance value can be found by applying a voltage source to the terminals, and calculating the current supplied.

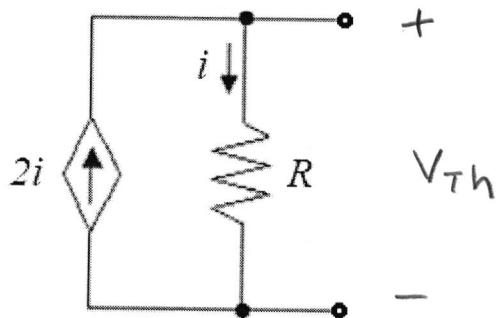


Answer 2:

Open Circuit:

$$2i - i = 0 \Rightarrow i = 0 \Rightarrow V_{TH} = 0$$

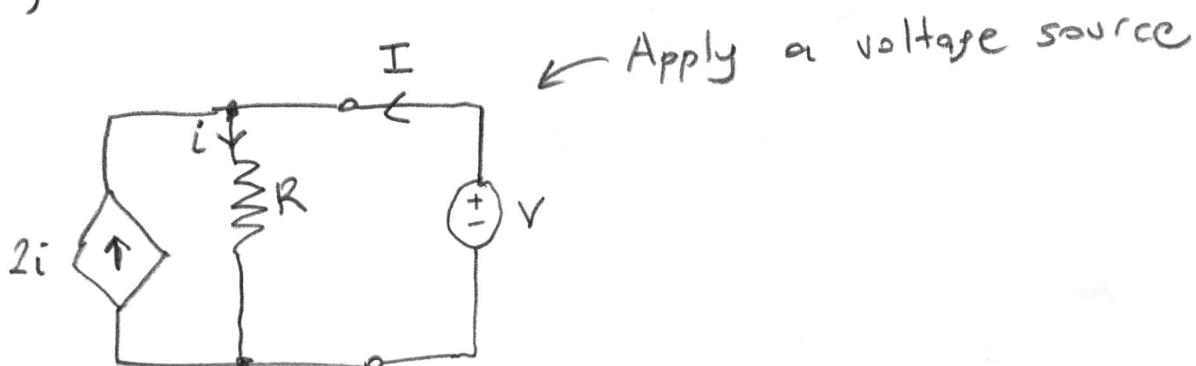\Rightarrow The circuit is equivalent to a pure resistance.



$$2i + I = i \Rightarrow i = -I$$

From Ohm's law: $V = i \cdot R$

$$\Rightarrow V = -I \cdot R$$

$$\Rightarrow \frac{V}{I} = -R \quad \leftarrow \text{The equivalent resistance value}$$

Therefore, the circuit is equivalent to:




\leftarrow Negative R resistance


(25 pts.) 3) A linear network N produces powers P_1 and P_2 when resistances R_1 and R_2 connected to it correspondingly. What should be the resistor value to obtain the maximum power from that network?

Hint: Use a Thevenin equivalent model for the circuit and find the parameters V_{TH} and R_{TH} using the given data.


Answer 3:

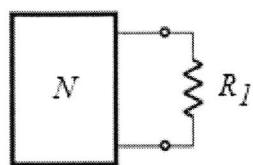

power: P_1

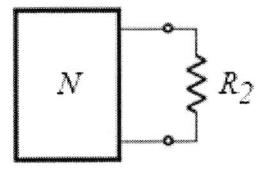

power: P_2

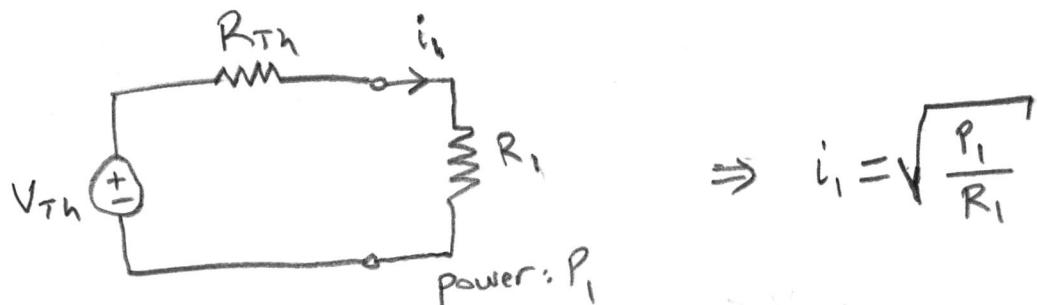

$$\Rightarrow i_1 = \sqrt{\frac{P_1}{R_1}}$$

$$\Rightarrow V_{TH} = (R_{TH} + R_1) \cdot \sqrt{\frac{P_1}{R_1}}$$

Similarly:


$$\Rightarrow V_{TH} = (R_{TH} + R_2) \cdot \sqrt{\frac{P_2}{R_2}}$$

If we equate these two equations, we obtain:

$$\Rightarrow R_{TH} = \frac{\sqrt{P_1 \cdot R_1} - \sqrt{P_2 \cdot R_2}}{\sqrt{P_2 / R_2} - \sqrt{P_1 / R_1}}$$

To obtain the maximum power, this resistor value should be used.

(25 pts.) 4) For the circuit shown, assume V_s value is known. Write four equations which are necessary to solve for the unknowns V_i , V_o , I_b , and I_o . Also, write an expression (in terms of the variables used) for the amount of power generated by the input voltage source V_s . **Do not** solve the equations; just write them correctly and completely.

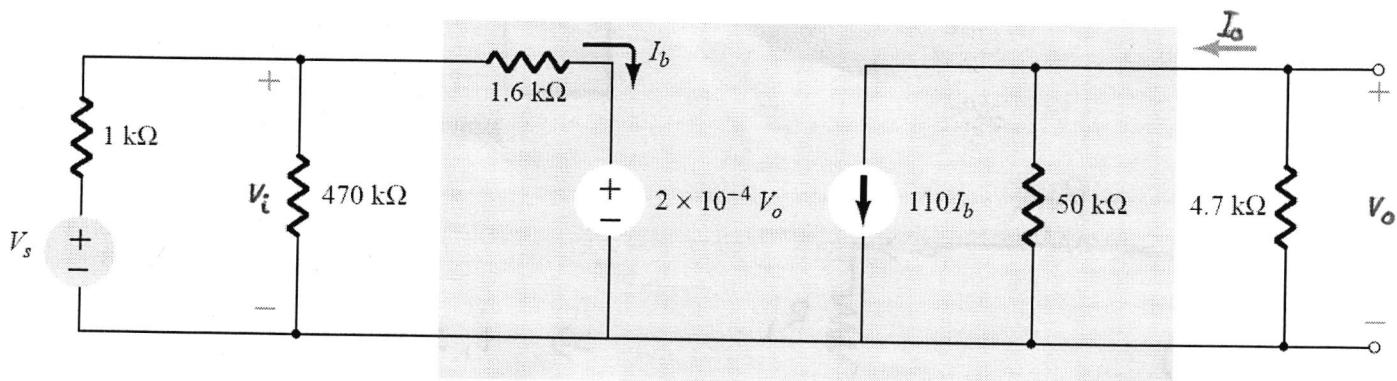

Equation 1:

$$\frac{V_i - V_s}{1K} + \frac{V_i}{470K} + \frac{V_i - 2 \cdot 10^{-4} V_o}{1.6K} = 0$$

Equation 2:

$$\frac{V_o}{4.7K} + \frac{V_o}{50K} + 110I_b = 0$$

Equation 3:

$$I_b = \frac{V_i - 2 \cdot 10^{-4} V_o}{1.6K}$$

Equation 4:

$$I_o = -\frac{V_o}{4.7K}$$

An expression for the power generated by the source V_s :

$$V_s \cdot \left(\frac{V_s - V_i}{1K} \right)$$