




Student Name: _____

EE201 Midterm Exam

Nov. 13, 2013


(30 pts.) 1) Consider the following circuit which models a long cable channel. Resistors repeat indefinitely. Note that the internal resistances are defined as $R_i = V_i/I_i$ for $i \geq 0$, and, $R_0 = R_1 = R_2 = \dots$

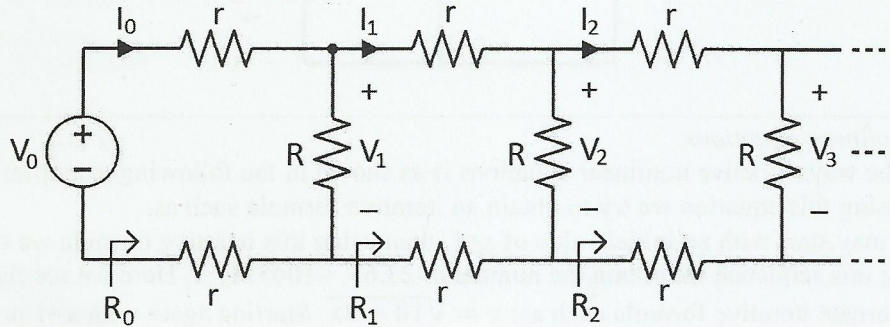- a) Find R_0 in terms of the resistance values r and R .
- b) Find the attenuation rate V_1/V_0 .



Hint: How to solve problems containing indefinitely repeating terms:
 Instead of a circuit example, let us consider a mathematical expression consisting of indefinitely repeating terms:
 $a = 1 + \frac{1}{1 + \frac{1}{1 + \dots}}$. Here, to solve for the value a , we need to notice that the same pattern repeats itself. We can write:
 $a = 1 + \frac{1}{a}$. From this last expression we can solve for a as: $a^2 = a + 1 \Rightarrow a = (1 \mp \sqrt{5})/2$. Since $a > 1$, $a = 1.618$, which is known to be the golden ratio. You may employ a similar strategy to solve the above problem.

Answer 1:

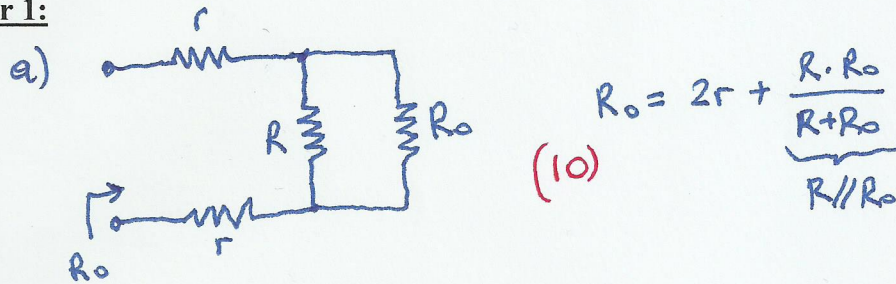

(10)
$$R_0 = 2r + \frac{R \cdot R_0}{R + R_0}$$

(5)
$$\Rightarrow R_0^2 - 2rR_0 - 2rR = 0$$

(5)
$$\Rightarrow R_0 = r + \sqrt{r^2 + 2rR}$$

b)
$$I_0 = \frac{V_0}{R_0}$$

(5)
$$V_1 = V_0 - 2r \cdot I_0 \quad \text{or} \quad V_1 = I_0 \cdot (R \parallel R_0)$$

(5)
$$\Rightarrow \frac{V_1}{V_0} = \frac{R}{R + R_0} = 1 - \frac{2r}{R_0}$$


$$\frac{V_1}{V_0} = \frac{R}{R + r + \sqrt{r^2 + 2rR}} = \frac{\sqrt{r^2 + 2rR} - r}{\sqrt{r^2 + 2rR} + r}$$

Note: Total time allowed is 110 min. Please show all your work and write legibly.

(20 pts.) 2) The following circuit contains a nonlinear element such that $I_d = 10^{-3}(e^{5V_d} - 1)$.

a) Obtain an equation containing only the variable V_d .

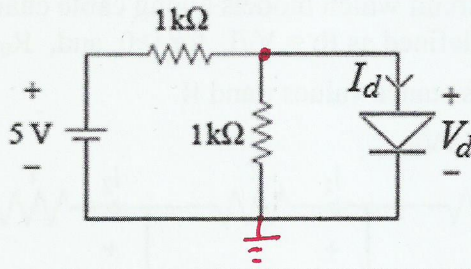b) Using the equation obtained in (a), find V_d within 5% error.



Hint: How to solve nonlinear equations:

Among many, one of the ways to solve nonlinear equations is as shown in the following example:

$3x + x^4 = 10$. Here, using this equation we try to obtain an iterative formula such as:

$x = (10 - x^4)/3$. We may start with an initial value of $x=1$, then using this iterative formula we obtain the next value as: $x=3$. Then repeating this sequence we obtain the numbers: -23.67, -104571, ... Here we see that it does not work!

Now we may try an alternate iterative formula such as: $x = \sqrt[4]{10 - 3x}$. Starting again with $x=1$ produces:

1.6266, 1.5043, 1.5305, 1.5250, 1.5262, 1.5259, 1.5260, 1.5260 ... Therefore we find the solution as $x=1.5260$.

Answer 2:

a) (9)
$$\frac{V_d - 5}{1000} + \frac{V_d}{1000} + I_d = 0$$

(5)
$$\Rightarrow 2V_d + e^{5V_d} - 6 = 0$$

b) (6)
$$V_d = 0.3347 \text{ V} \quad (0.31 \dots 0.36 \text{ ok.})$$

$$I_d = 4.3306 \text{ mA}$$


(using $V_d \leftarrow \frac{1}{5} \ln(6 - 2V_d)$)

(25 pts.) 3) A power generating linear circuit produces 720 W when 5 Ohms or 20 Ohms connected to it. What is the maximum power that could be obtained from such generator? Which resistor value must be used for that?

Hint:

Use a Thevenin equivalent model for the circuit and find the parameters V_{TH} and R_{TH} using the given data.

Answer 3:

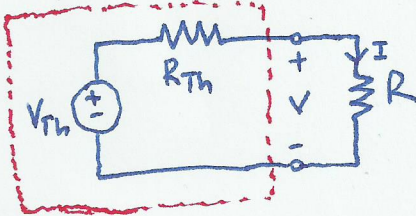

5 Ω Connected:

$$P_R = \frac{V^2}{R} = I^2 R$$

$$\Rightarrow V = \sqrt{720 \cdot 5} = 60 \text{ V}$$

$$I = \sqrt{\frac{720}{5}} = 12 \text{ A}$$

$$\Rightarrow V_{TH} = R_{TH} \cdot I + V$$

$$(6) \quad \underline{V_{TH} = R_{TH} \cdot 12 + 60}$$

20 Ω Connected

$$V = \sqrt{720 \cdot 20} = 120 \text{ V}$$

$$I = \sqrt{\frac{720}{20}} = 6 \text{ A}$$

$$(6) \Rightarrow \underline{V_{TH} = R_{TH} \cdot 6 + 120}$$

or:

$$P_R = \left(\frac{V_{TH}}{R_{TH} + R} \right)^2 \cdot R$$

$$(6) \Rightarrow R_{TH} = 10 \Omega$$


$$V_{TH} = 180 \text{ V}$$

(3) To get the maximum power $R = R_{TH} = 10 \Omega$

$$\Rightarrow V_{\max} = \frac{V_{TH}}{2} = 90 \text{ V}$$

$$(4) \Rightarrow P_{R \max} = \frac{90^2}{10} = \underline{\underline{810 \text{ W}}}$$

(25 pts.) 4) For the circuit shown, write five equations which are necessary to solve for the unknowns V_1 , V_2 , V_3 , i_B , and i_1 . Do not solve the equations; just write them correctly and completely.

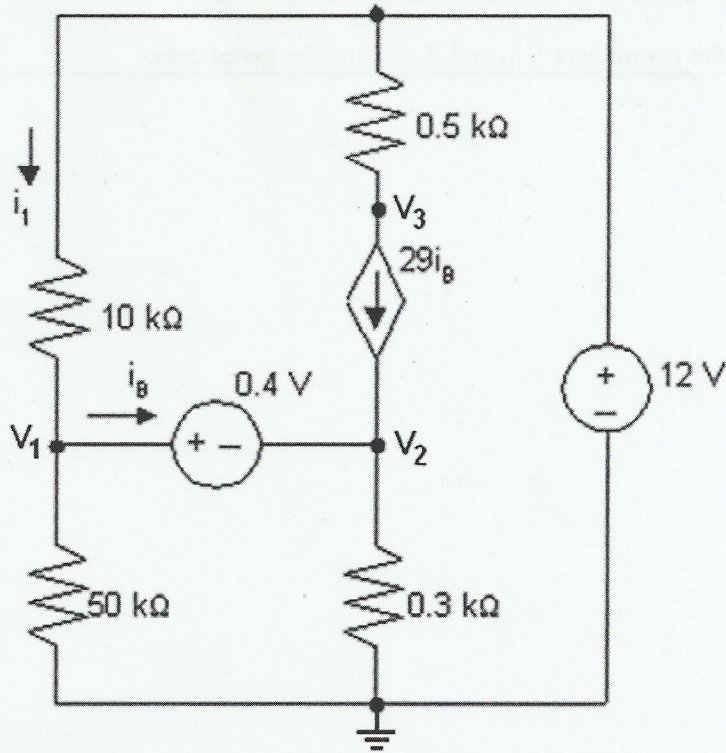

Equation 1:

$$(5) \quad \frac{V_1}{50K} + \frac{V_1 - 12}{10K} + i_B = 0$$

Equation 2:

$$(5) \quad \frac{V_2}{0.3K} - i_B - 29i_B = 0$$

Equation 3:

$$(5) \quad \frac{V_3 - 12}{0.5K} + 29i_B = 0$$

Equation 4:

$$(5) \quad V_1 - V_2 = 0.4$$

Equation 5:

$$(5) \quad \frac{12 - V_1}{10K} = i_1$$