





Student Name: _____

EE201 Quiz

Dec. 09, 2013

(40 pts.) 1) Consider the circuit given.

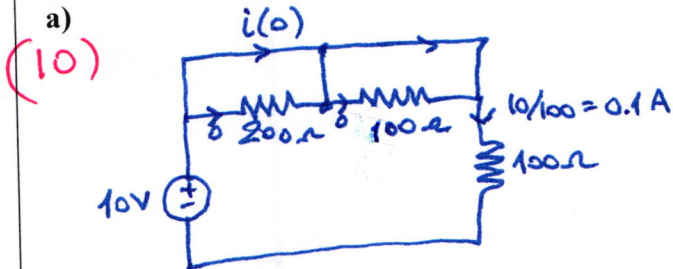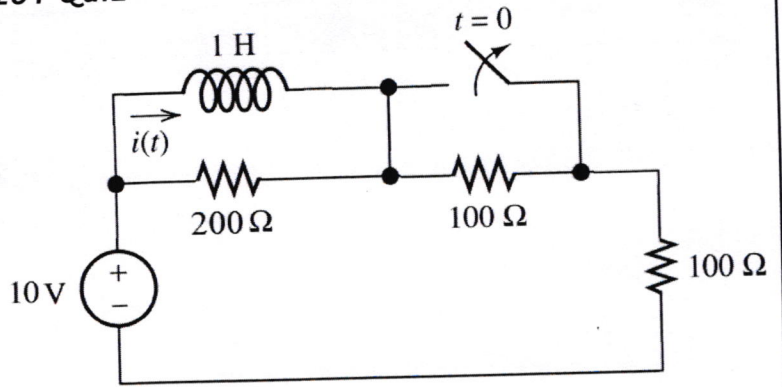- Find the initial current $i(0)$.
 - Find the differential equation of $i(t)$ for $t \geq 0$.
 - Solve the differential equation and find $i(t)$.
 - Sketch $i(t)$ for $t \geq 0$.
- (Please show all important aspects and units)




$\Rightarrow i(0) = 0.1 \text{ A}$

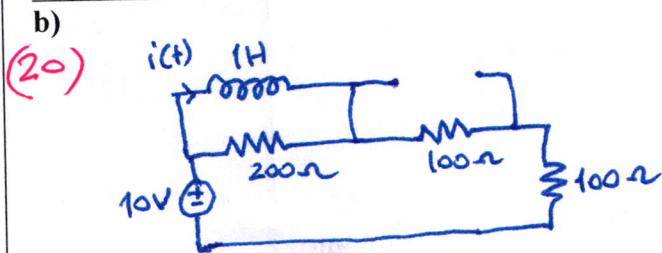v. wr $\rightarrow -8$
w/answer

switch wrong $\rightarrow -5$

wr $\rightarrow -5$
little math $\rightarrow -2$



$\Rightarrow 10 = 1 \cdot \frac{di}{dt} + 200 \cdot (i(t) + \frac{1}{200} \frac{di}{dt})$

$\Rightarrow \frac{di}{dt} + 100i = 5$

1wr $\rightarrow -8$

≥ 2 wr, v. wrong $\rightarrow -15$

c)

(5)

$i(t) = (0.1 - \frac{5}{100}) e^{-100t} + \frac{5}{100}$


$\Rightarrow i(t) = 0.05 e^{-100t} + 0.05 \text{ (A)}$

$\tau = \frac{1}{a} = \frac{1}{100} = 0.01 \text{ sec.}$

v. wr $\rightarrow -5$


wr. with $e \rightarrow -3$

little math wr $\rightarrow -2$

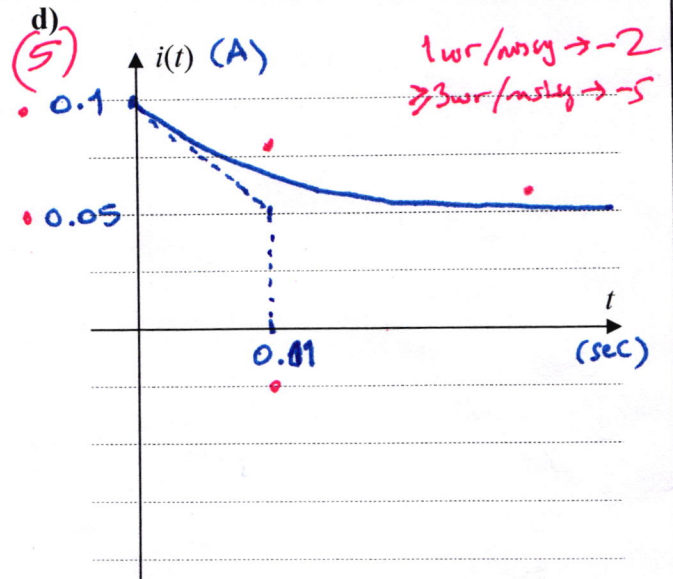

Note: Total time allowed is 75 min. Please show all your work and write legibly.

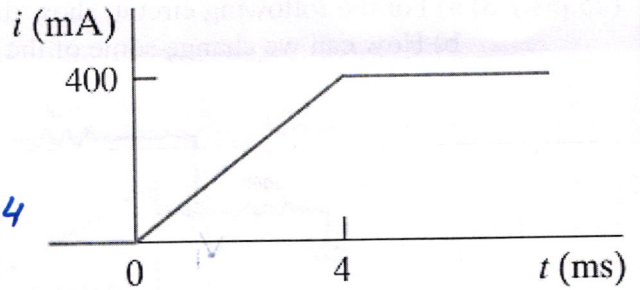(35 pts.) 2) The current shown is applied to the following components. Find the expression of the corresponding voltage for each case, and draw it carefully.




$$i = \begin{cases} 0 & t < 0 \\ 100t & 0 \leq t \leq 0.004 \\ 0.4 & t > 0.004 \end{cases}$$

Answer 2:

a) 10Ω Resistance

(6)

$$V = R \cdot i = 10 \cdot i$$

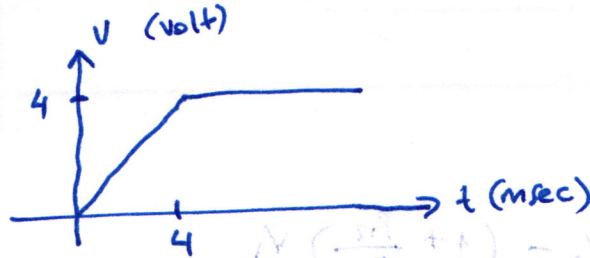

Exp. Draw

	$t < 0$	$0 < t < 4$	$t > 4$
Exp.	1	1	1
Draw	1	1	1

b) $10 \mu\text{F}$ Capacitance


(17)

$$V = \frac{1}{10 \cdot 10^{-6}} \int_{-\infty}^t i dt$$

For $t \leq 0 \Rightarrow V(t) = 0$

For $0 < t < 0.004 \Rightarrow V(t) = 10^5 \cdot \int_0^t 100t dt = 5 \cdot 10^6 t^2$

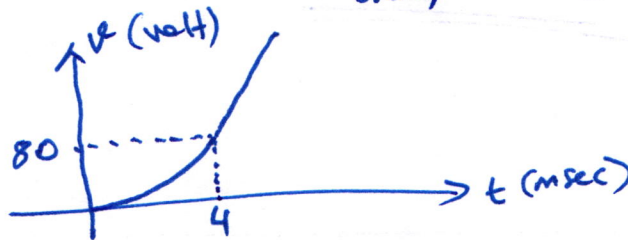For $t > 0.004 \Rightarrow V(t) = 10^5 \cdot \int_{0.004}^t 0.4 dt + 80 = 40 \cdot 10^3 \cdot (t - 0.004) + 80 = 40 \cdot 10^3 t - 80$




Exp. Draw

	1	$6/2$	$4/2$
Draw	1	3	2

c) 10 mH Inductance

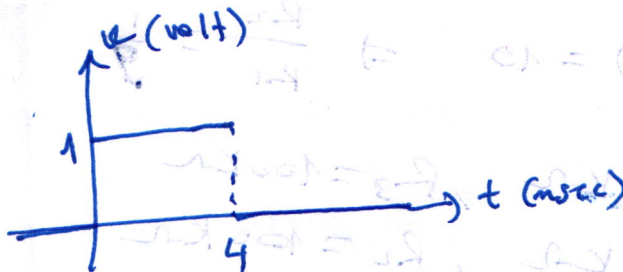(12)

$$V = 10 \cdot 10^{-3} \frac{di}{dt} = \begin{cases} 0 & t < 0 \\ 1 & 0 \leq t \leq 0.004 \\ 0 & t > 0.004 \end{cases}$$




Exp. Draw

	1	$4/2$	2
Draw	1	2	2

(25 pts.) 3) a) For the following circuit, show that $V_o = 2(V_2 - V_1)$.

b) How can we change some of the resistor values to make the difference gain as 10?

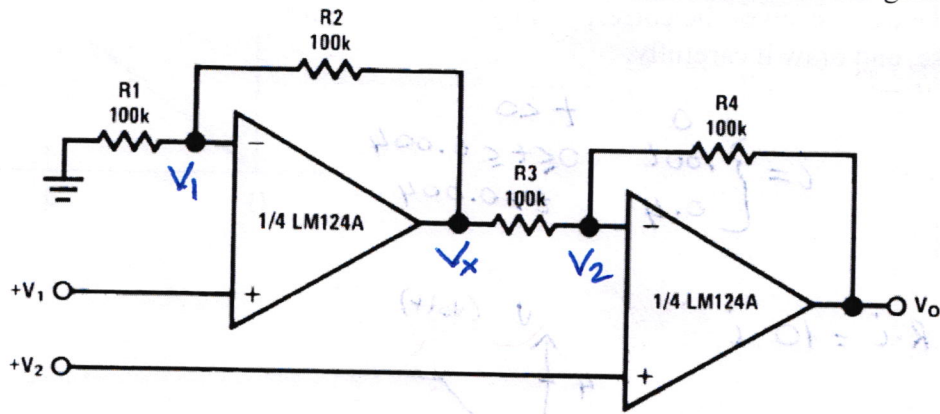

Answer 3:

a)

(10) $V_x = \left(1 + \frac{R_2}{R_1}\right) V_1$

$$\frac{V_2 - V_x}{R_3} + \frac{V_2 - V_o}{R_4} = 0$$

$$\Rightarrow V_o = V_2 \cdot \left(1 + \frac{R_4}{R_3}\right) - \frac{R_4}{R_3} V_x$$

$$\Rightarrow V_o = V_2 \cdot \left(1 + \frac{R_4}{R_3}\right) - \frac{R_4}{R_3} \cdot \left(1 + \frac{R_2}{R_1}\right) V_1$$

$$\Rightarrow V_o = \underline{\underline{2 \cdot V_2 - 2 \cdot V_1}}$$

Δ	Δ	1	9×3
Δ	Δ	1	9×3

b)

(15)

$$1 + \frac{R_4}{R_3} = 10 \Rightarrow \frac{R_4}{R_3} = 9$$

$$\frac{R_4}{R_3} \left(1 + \frac{R_2}{R_1}\right) = 10 \Rightarrow \frac{R_2}{R_1} = \frac{1}{9}$$

Choose $\Rightarrow R_4 = 900 \text{ k}\Omega, R_3 = 100 \text{ k}\Omega$
 $R_1 = 900 \text{ k}\Omega, R_2 = 100 \text{ k}\Omega$

v. little or w/ dead point $\rightarrow 10$
 only result with points only