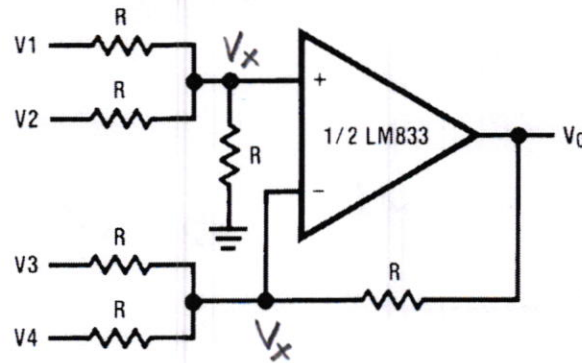


Student Name: _____

EE201 Midterm Exam #1

Dec. 5, 2017

(25 pts.) 1) Find the output voltage V_o in terms of the input voltages V_1 , V_2 , V_3 , and V_4 .



Answer 1:

$$\frac{V_x - V_1}{R} + \frac{V_x - V_2}{R} + \frac{V_x}{R} = 0$$

$$\Rightarrow V_x = \frac{V_1 + V_2}{3}$$

$$\frac{V_x - V_3}{R} + \frac{V_x - V_4}{R} + \frac{V_x - V_o}{R} = 0$$



$$\Rightarrow \underline{\underline{V_o = V_1 + V_2 - V_3 - V_4}}$$

(40 pts.) 2) Consider the circuit given.

- Find the initial current $i(0)$.
- Find the differential equation of $i(t)$ for $t \geq 0$.
- Solve the differential equation and find $i(t)$.
- Sketch $i(t)$ for $t \geq 0$.


(Please show all important aspects and units)

a)

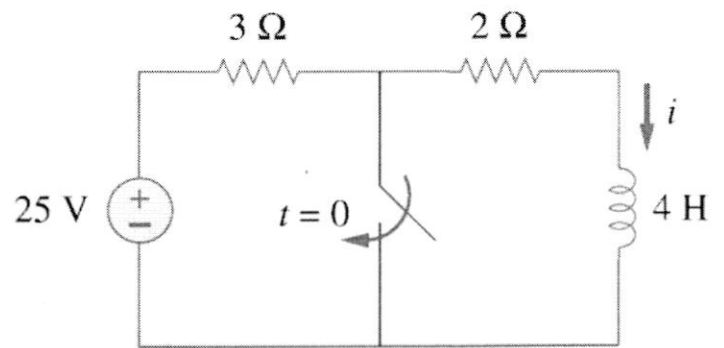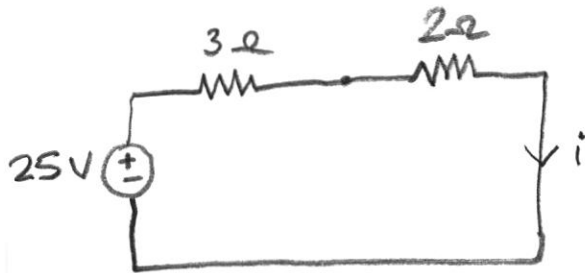

$$\Rightarrow i(0) = \frac{25}{3+2} = 5 \text{ A}$$

b)

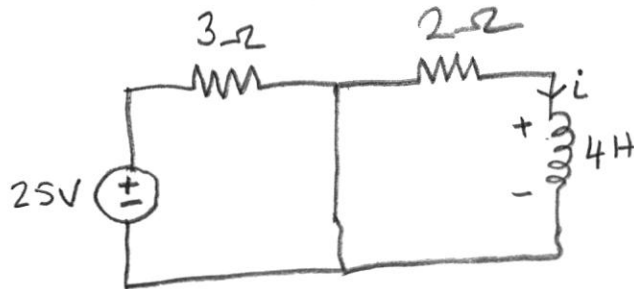


$$4 \frac{di}{dt} + 2i = 0$$

$$\Rightarrow \frac{di}{dt} + 0.5i = 0$$


c)

$$i(t) = 5 \cdot e^{-t/2}$$

d)

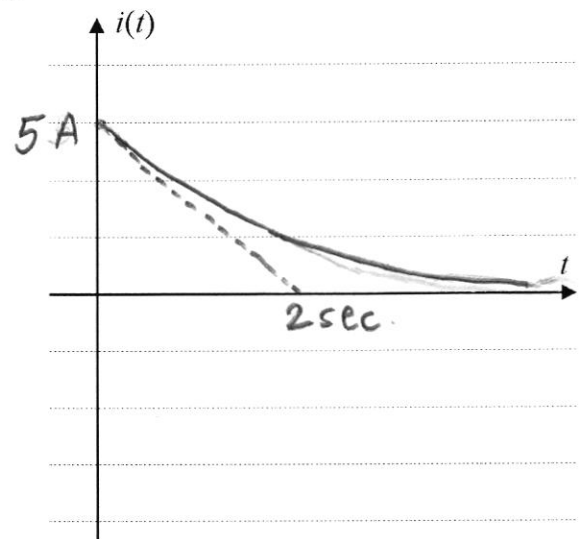

(35 pts.) 3) Second order Low Pass Filter (Butterworth) circuit is shown below. Write Node Voltage Analysis equations as necessary. Find a differential equation involving only V_I and V_O voltages.

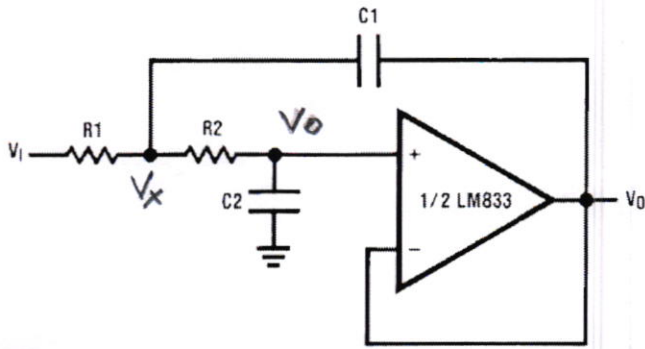

Answer 3:

$$\frac{V_x - V_I}{R_1} + \frac{V_x - V_O}{R_2} + C_1 \frac{d(V_x - V_O)}{dt} = 0$$

$$\frac{V_O - V_x}{R_2} + C_2 \frac{dV_O}{dt} = 0$$

$$\Rightarrow V_x = R_2 C_2 \frac{dV_O}{dt} + V_O$$

$$\Rightarrow \frac{d(V_x - V_O)}{dt} = R_2 C_2 \frac{d^2 V_O}{dt^2} + \frac{dV_O}{dt}$$

$$\Rightarrow \left(\frac{1}{R_1} + \frac{1}{R_2} \right) (R_2 C_2 \frac{dV_O}{dt} + V_O) - \frac{V_I}{R_1} - \frac{V_O}{R_2} + C_1 R_2 C_2 \frac{d^2 V_O}{dt^2} = 0$$

$$\Rightarrow \underline{\underline{C_1 C_2 R_1 R_2 \frac{d^2 V_O}{dt^2} + (R_1 + R_2) C_2 \frac{dV_O}{dt} + V_O = V_I}}$$