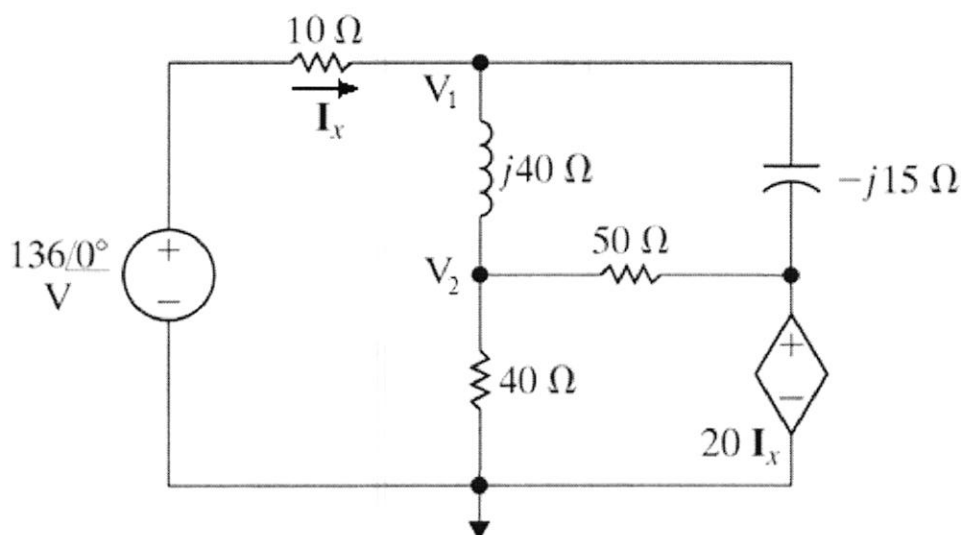


Student Name: _____

EE201 Midterm Exam #2

Jan. 9, 2018

(30 pts) 1) Write the necessary equations for solving the node voltages V_1 and V_2 ; and, the current I_x in the following AC circuit. **Do not** solve the equations; just write them correctly and completely.



Equation 1:

$$\frac{V_1 - 136}{10} + \frac{V_1 - V_2}{j40} + \frac{V_1 - 20I_x}{-j15} = 0$$

Equation 2:


$$\frac{V_2 - V_1}{j40} + \frac{V_2 - 20I_x}{50} + \frac{V_2}{40} = 0$$

Equation 3:

$$I_x = \frac{136 - V_1}{10}$$

Note: Total time allowed is 100 min. Please show all your work and write legibly.

(30 pts) 2) For the second order Butterworth circuit below, find the transfer function $H(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)}$

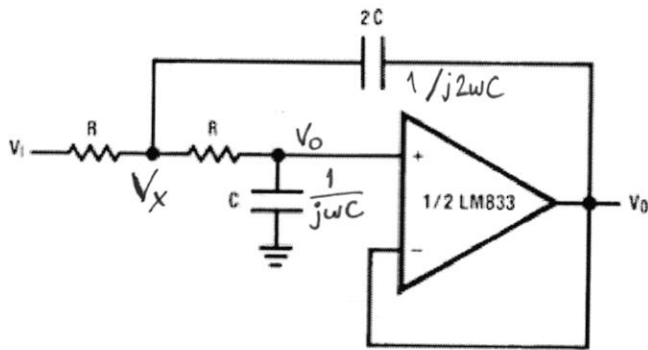

Answer 2:

$$\frac{V_x - V_i}{R} + \frac{V_x - V_o}{R} + (V_x - V_o) \cdot j2\omega C = 0$$


$$\frac{V_o - V_x}{R} + V_o \cdot j\omega C = 0$$

$$\Rightarrow V_x = V_o \cdot (1 + j\omega RC)$$


$$\Rightarrow V_o(1 + j\omega RC) - V_i + V_o j\omega RC + V_o j\omega RC \cdot j2\omega RC = 0$$

$$\Rightarrow H = \frac{V_o}{V_i} = \frac{1}{(j\omega)^2 \cdot 2R^2C^2 + j\omega 2RC + 1}$$

(40 pts) 3) For the following AC circuit, find the voltage $v_C(t)$, and, the average, reactive and apparent power delivered by the voltage source.

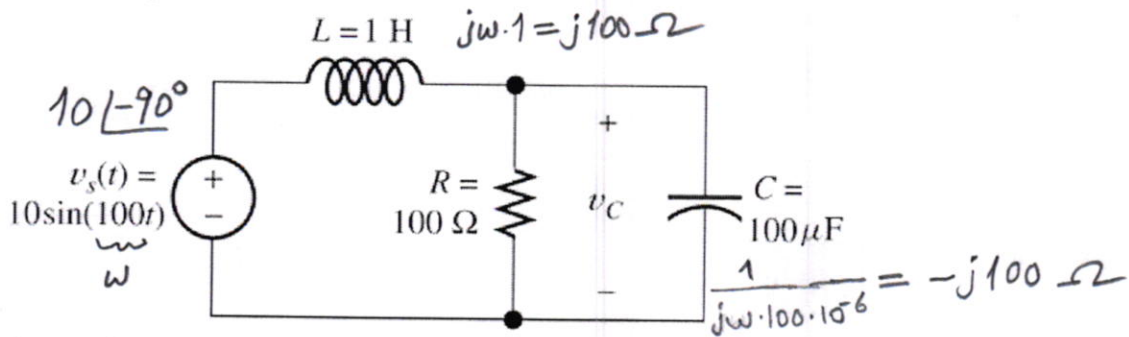

Answer 3:

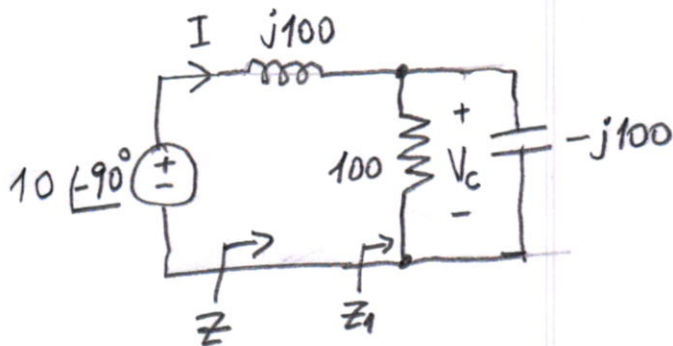

$$Z = j100 + \frac{1}{\frac{1}{100} + \frac{1}{100j}} = j100 + \underbrace{50 - j50}_{Z_1} = \underline{\underline{50 + j50 \Omega}}$$

$$\Rightarrow I = \frac{-10j}{50 + j50} = \underline{\underline{-0.1 - 0.1j \text{ A}}}$$

$$\Rightarrow V_C = I \cdot Z_1 = (-0.1 - 0.1j)(50 - j50) = \underline{\underline{-10 \text{ V}}}$$

$$\Rightarrow \underline{\underline{v_C(t) = 10 \cdot \cos(100t - 180^\circ)}}$$

$$S = \frac{1}{2} V_s I^* = 0.5 \times (-10j) \times (-0.1 + 0.1j) = 0.5 + 0.5j \text{ VA}$$

$$\text{Average Power} = 0.5 \text{ W}$$

$$\text{Reactive Power} = 0.5 \text{ VAR}$$

$$\text{Apparent Power} = 0.707 \text{ VA}$$