



MARMARA UNIVERSITY
FACULTY OF ENGINEERING

PHYS 1104
PHYSICS LABORATORY II

Capacitor Charge and Discharge

Section:

Group:

Instructor:

Date:

	Department	Student Id Number	Name & Surname
1			
2			
3			

1 Purpose

To observe the effects of capacitance, resistance and voltage on the charging of a capacitor in an RC circuit .

2 Theory

Basically a capacitor can be built by placing two metal conductive plate face to face in a small distance. Then the plates are connected to a voltage source and when the potential is applied one of the plates are charged (+) Q ,while other is (-) Q. The voltage difference between the two plates are approximately V applied potential. Capacitance is the ratio of the charge to the potential difference between the plates. It is shown by “C” with a unit of Farad (F) which is in SI unit system. Capacitance of the capacitor:

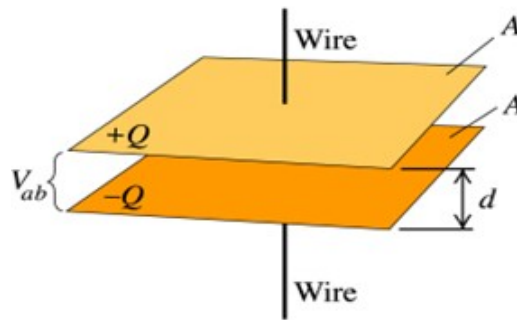


Figure 1: Example of parallel plate and cylindrical capacitors with the one that is used during the experiment

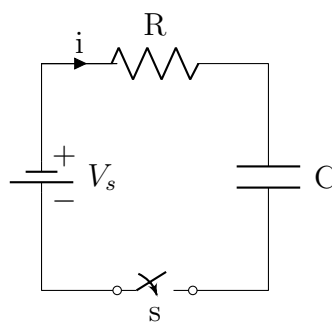


Figure 2: Capacitor charging circuit diagram

The relation of current and voltage with time $I(t)$ (Figure 2), when a capacitor which has a capacitance of C is charged through a resistor R at a fixed voltage V is given by

$$I(t) = \frac{V_s}{R} e^{-\frac{t}{RC}} \quad (1)$$

$$V_c = V_s(1 - e^{-\frac{t}{RC}}) \quad (2)$$

Here, V_s is the source voltage, R is the resistance, V_c is the voltage on capacitor and the product of RC is named as the time constant (τ). The dependence of the current on the capacitance, the resistance and the voltage should be worked out by systematically varying these parameters. In the case of discharging of the capacitor the relation can be seen below

$$I(t) = -\frac{V_s}{R}e^{-t/RC} \quad (3)$$

$$V_c = V_s e^{-t/RC} \quad (4)$$

3 Experimental Setup

3.1 Equipment List

1. Board x1
2. Dc voltage source x1
3. Digital multimeter x2
4. Capacitor x2
5. Resistor x1
6. Connection cables x9

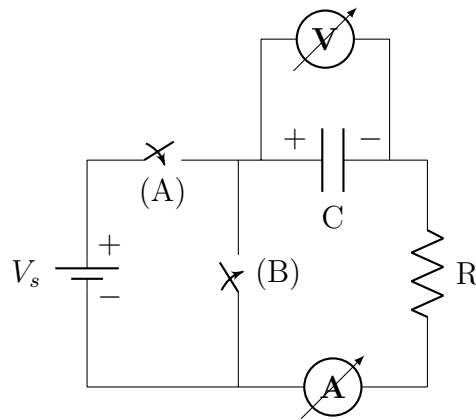


Figure 3: Circuit diagram

The experimental setup is shown in Figure 3. The internal resistance of the digital multimeter and the setting time can be disregarded. R is a protective resistor that limits the current while discharging (Switch setting B) the capacitor.

In this experiment, you will record the voltage across the capacitor and current passing through the circuit as a function of time for various capacitance and voltage source values. To observe the theoretical relation given in Eq. 1, it is best to graph natural logarithm of the current as a function of time. In that case, the theoretical expression can be written as

$$\ln I = \ln \left(\frac{V}{R} \right) - \frac{1}{RC} t \quad (5)$$

Therefore, in the graph the slope is $-\frac{1}{RC}$ and the y intercept is $\ln(V/R)$. Using the slope of the graph, time constant of the circuit can be easily calculated.

4 Procedure

1. Ensure that the capacitor and resistance are working properly. Check with multimeter.
2. Adjust the voltage source to the desired value precisely and ensure that it works correctly using a digital multimeter.
3. Build the circuit shown in Figure 3 but be careful the minus part of the capacitor should be plugged in the correct direction of the current. If it is plugged in a wrong way the circuit does not work as requested.

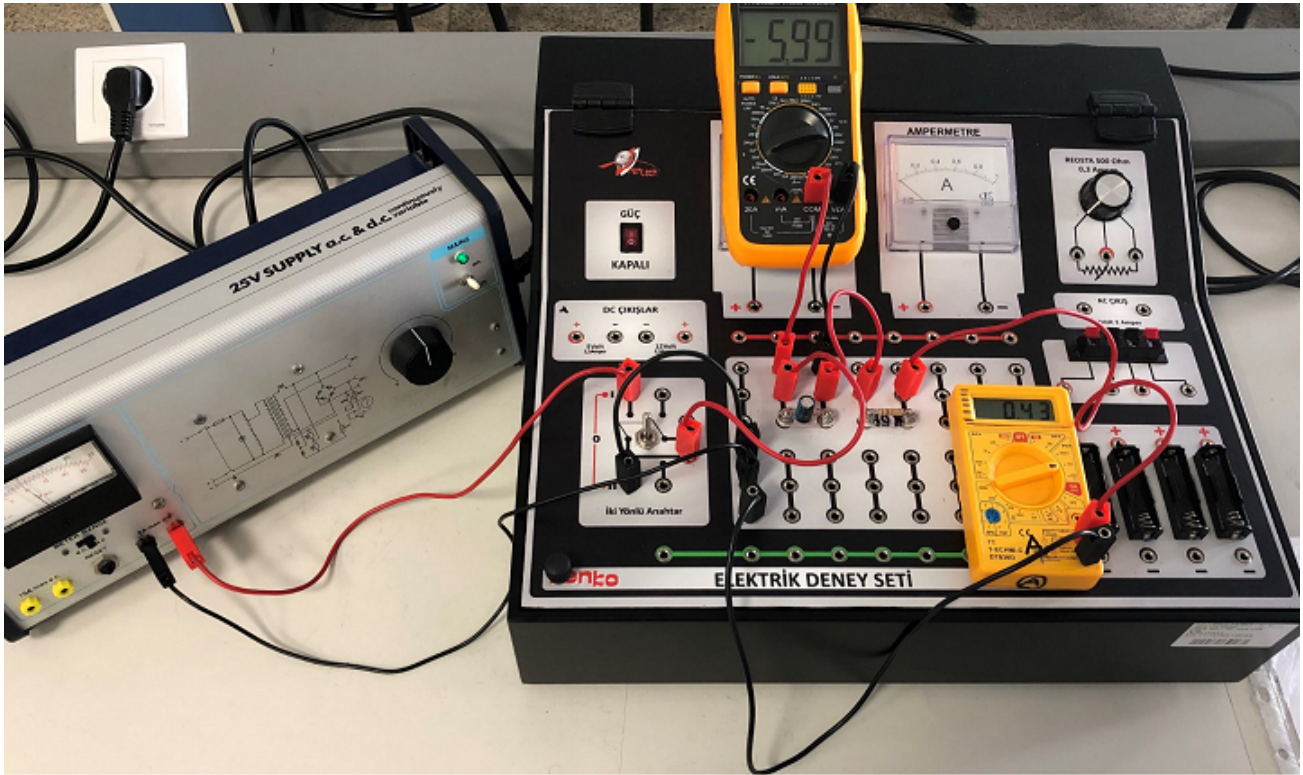


Figure 4: Experiment setup

Capacitor Charge and Discharge

Part I

By using the multimeter and the chronometer, record the experimental voltage value of the capacitor and current passing through the circuit as a function of time using the capacitor $C_1 = 1000 \mu\text{F}$ and resistance $R = 10 \text{ k}\Omega$. Set the voltage source to $V_s = 10\text{V}$. (In the case of charging that means switch A is closed when switch B is opened).

NOTE: First, ensure that the capacitor is fully discharged by changing the switch to the position of II (position II corresponds to the closure of switch B in Figure 3).

Time (s)	I_{exp} (mA)	V_c (Volt)	Time (s)	I_{exp} (mA)	V_c (Volt)	Time (s)	I_{exp} (mA)	V_c (Volt)
5			115			225		
10			120			230		
15			125			235		
20			130			240		
25			135			245		
30			140			250		
35			145			255		
40			150			260		
45			155			265		
50			160			270		
55			165			275		
60			170			280		
65			175			285		
70			180			290		
75			185			295		
80			190			300		
85			195			305		
90			200			310		
95			205			315		
100			210			320		
105			215			325		
110			220			330		

Capacitor Charge and Discharge

Part II

Repeat the same procedure in Part I when switch B is closed and switch A is opened. It is called as discharging of the capacitor.

Time (s)	I_{exp} (mA)	V_c (Volt)	Time (s)	I_{exp} (mA)	V_c (Volt)	Time (s)	I_{exp} (mA)	V_c (Volt)
5			115			225		
10			120			230		
15			125			235		
20			130			240		
25			135			245		
30			140			250		
35			145			255		
40			150			260		
45			155			265		
50			160			270		
55			165			275		
60			170			280		
65			175			285		
70			180			290		
75			185			295		
80			190			300		
85			195			305		
90			200			310		
95			205			315		
100			210			320		
105			215			325		
110			220			330		

Capacitor Charge and Discharge

Part III

By using the multimeter and the chronometer, record the experimental voltage value of the capacitor and current passing through the circuit as a function of time using the capacitor $C_2 = 2200 \mu\text{F}$ or make parallel connection of two capacitors of $1000 \mu\text{F}$ where the equivalent capacitance will be doubled as $2000 \mu\text{F}$ and the resistance $R = 10 \text{ k}\Omega$. Set the voltage source to $V_s = 10\text{V}$. (In the case of charging that means switch A is closed when switch B is opened)

Time (s)	I _{exp} (mA)	V _c (Volt)	Time (s)	I _{exp} (mA)	V _c (Volt)	Time (s)	I _{exp} (mA)	V _c (Volt)
5			115			225		
10			120			230		
15			125			235		
20			130			240		
25			135			245		
30			140			250		
35			145			255		
40			150			260		
45			155			265		
50			160			270		
55			165			275		
60			170			280		
65			175			285		
70			180			290		
75			185			295		
80			190			300		
85			195			305		
90			200			310		
95			205			315		
100			210			320		
105			215			325		
110			220			330		

Part IV


By using the multimeter and the chronometer, record the experimental voltage value of the capacitor and current passing through the circuit as a function of time using the capacitor $C_1 = 1000 \mu\text{F}$ and the resistance $R = 10 \text{ k}\Omega$. Set the voltage source to $V_s = 5\text{V}$. (In the case of charging that means switch A is closed when switch B is opened)

Time (s)	I_{exp} (mA)	V_c (Volt)	Time (s)	I_{exp} (mA)	V_c (Volt)	Time (s)	I_{exp} (mA)	V_c (Volt)
5			115			225		
10			120			230		
15			125			235		
20			130			240		
25			135			245		
30			140			250		
35			145			255		
40			150			260		
45			155			265		
50			160			270		
55			165			275		
60			170			280		
65			175			285		
70			180			290		
75			185			295		
80			190			300		
85			195			305		
90			200			310		
95			205			315		
100			210			320		
105			215			325		
110			220			330		

- Plot voltage vs time graph. How does the volage across the capacitor change with the time for all cases?
- Plot (I_{exp}) vs time graph. How does the current change with the time for all cases?
- Calculate the theoretical values of the time constants (RC) for all cases. Determine the experimental values of the time constants by drawing the $\ln(I_{exp})$ vs time graph. In order to do that, calculate the $\ln()$ values with calculator first. The slope of the graph will be $(-1/RC)$ which is shown in Equation 5. After mathematical manipulation, determine the percentage error in time constant.

Capacitor Charge and Discharge

graph paper

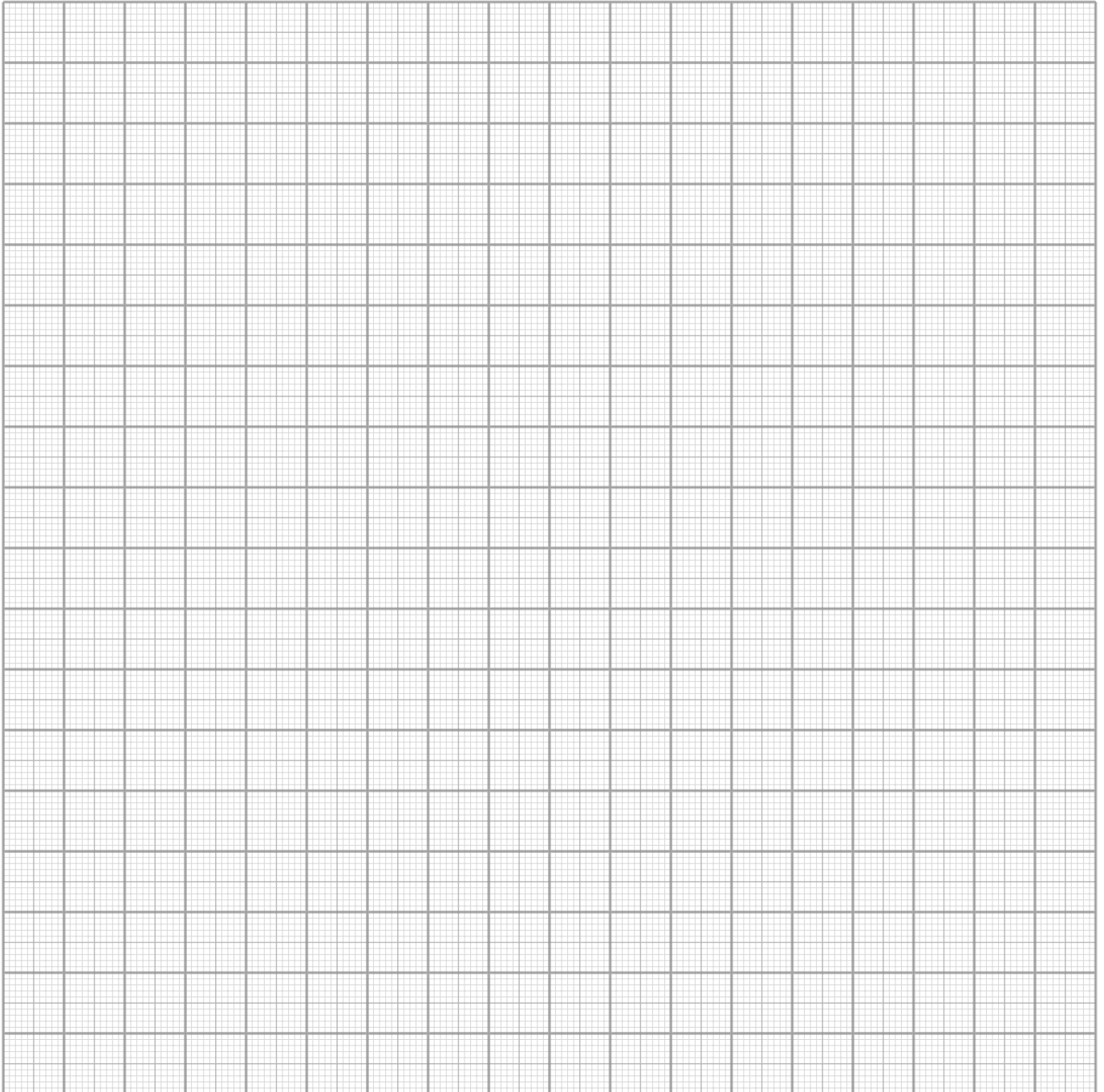

Time constant for	Theoretical	Experimental
C_1 :
C_2 :

% percentage error for C_1
C_2

7. How does the time constant change as the capacitance in the circuit increases?